

# **PSIM: A Tutorial**


# Presentation Outline

- **What is PSIM?**
- **Circuit Structure**
- **Getting started with PSIM**
- **Hands-on Examples**

# What is PSIM?

- PSIM is a simulation package specifically designed for power electronics and control circuits.
- Manufactured by Powersim Inc.  
( [www.powersimtech.com](http://www.powersimtech.com) )
- It allows fast simulation and it has a friendly user interface.
- PSIM is indicated for system-level simulation, control loop design and motor drive system studies.
- The basic PSIM package consists of three programs: circuit schematic program (**SIMCAD**), simulator program (**PSIM**), and waveform display program (**SIMVIEW**).

# Circuit Structure

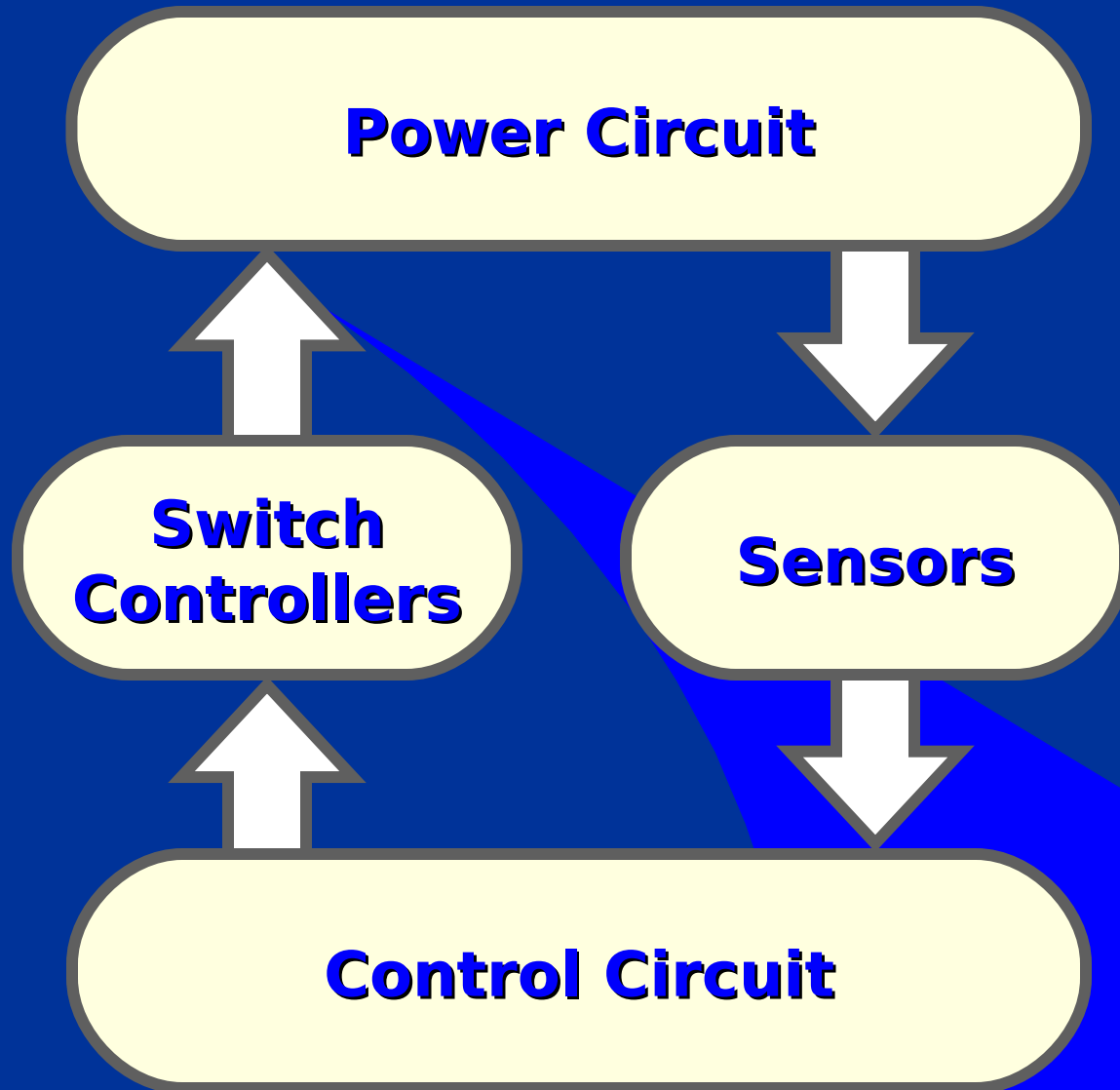


# Circuit Structure

<b>Power Circuit</b>	<b>Control Circuit</b>	<b>Switch Controllers</b>	<b>Sensors</b>
<ul style="list-style-type: none"><li>➤ <b>Switching devices</b></li><li>➤ <b>RLC branches</b></li><li>➤ <b>Transformers</b></li><li>➤ <b>Coupled inductors</b></li></ul>	<ul style="list-style-type: none"><li>➤ <b>S-domain blocks</b></li><li>➤ <b>Z-domain blocks</b></li><li>➤ <b>Logic components</b></li><li>➤ <b>Non-linear components</b></li></ul>	<ul style="list-style-type: none"><li>➤ <b>On-Off controllers</b></li><li>➤ <b>PWM controllers</b></li><li>➤ <b>Alpha controllers</b></li></ul>	<ul style="list-style-type: none"><li>➤ <b>Current</b></li><li>➤ <b>Voltage</b></li><li>➤ <b>Torque</b></li><li>➤ <b>Speed</b></li></ul>

# Getting Started with PSIM

- Start PSIM: go to *c:\PSIM6\_DEMO -> PSIM*

**New  
circuit**

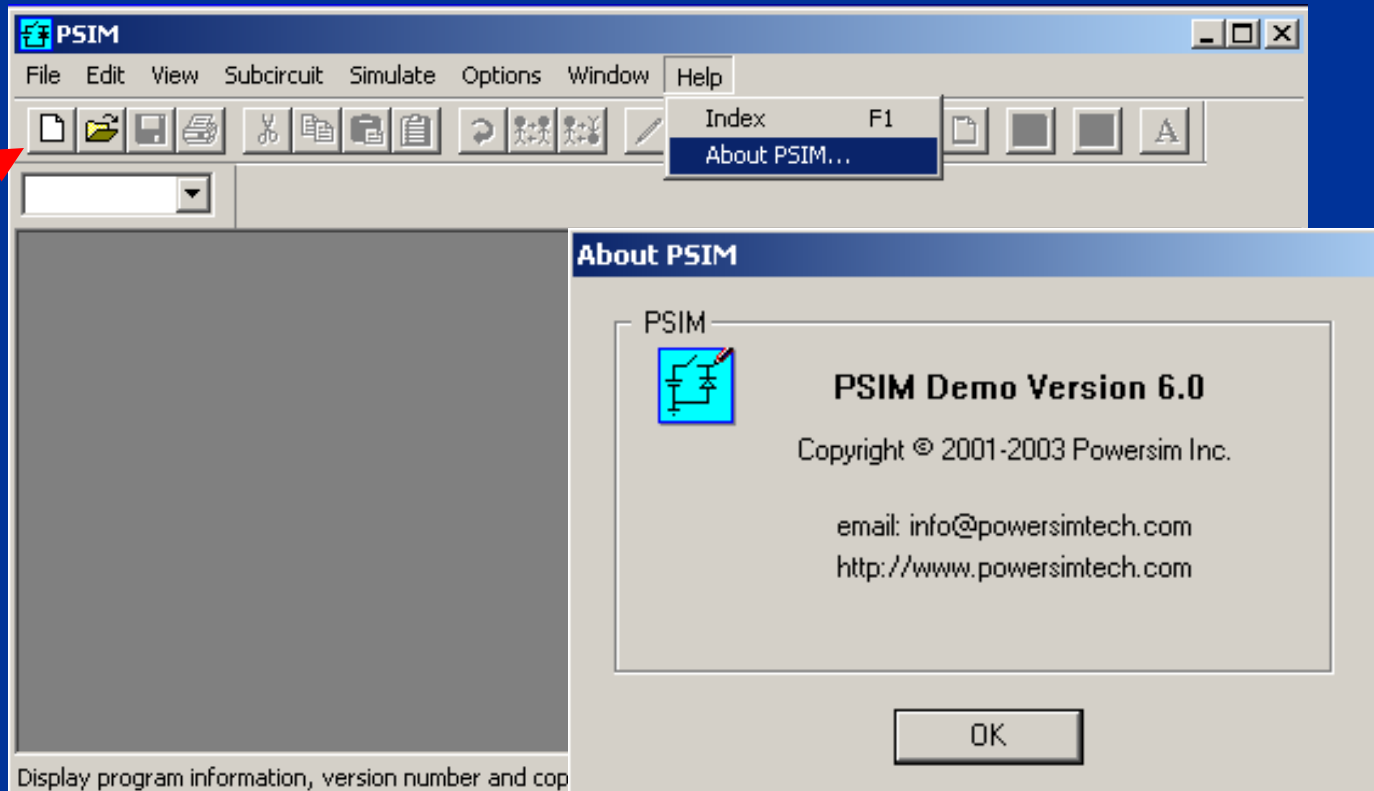


# Getting Started with PSIM

- Create a new circuit

**Menu**

**Toolbar**

**Circuit window**

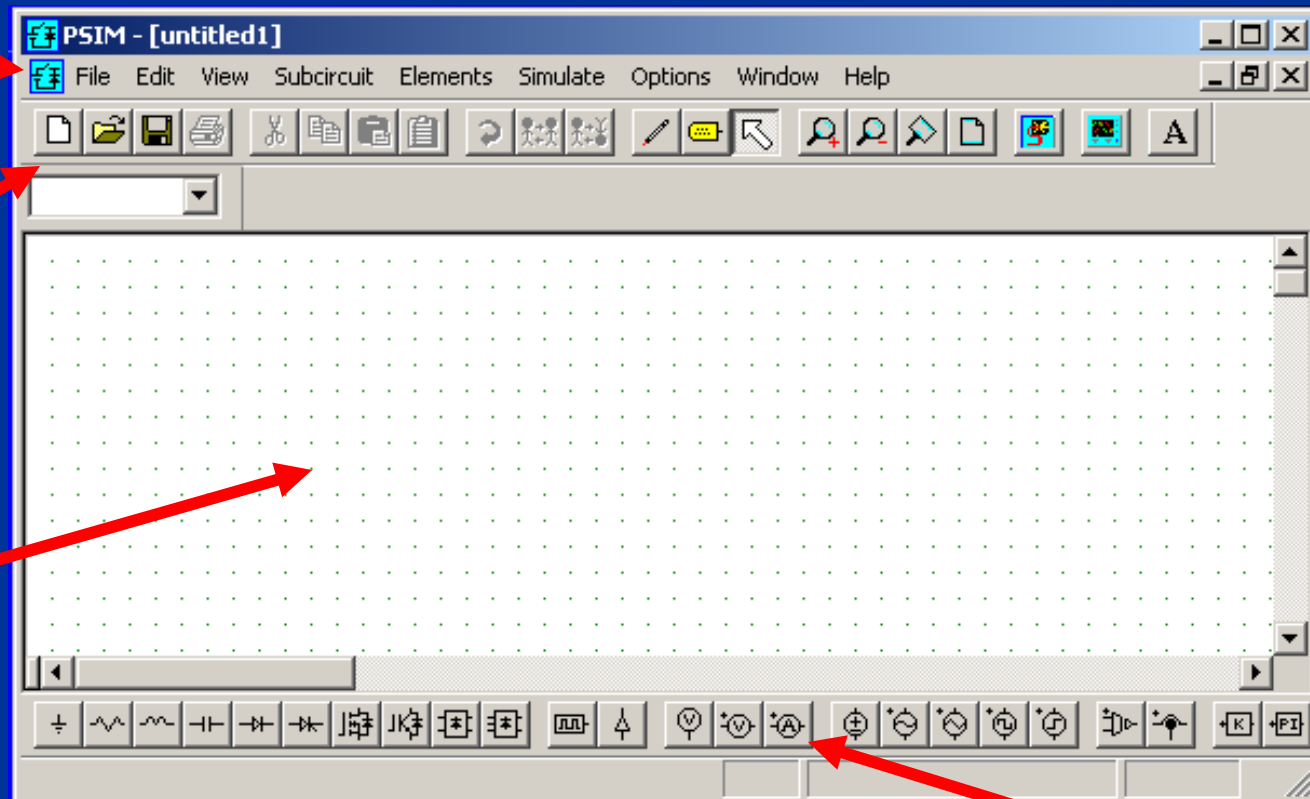


**Element  
toolbar**

# Getting Started with PSIM

## Example 1 – 1st Order System


### System

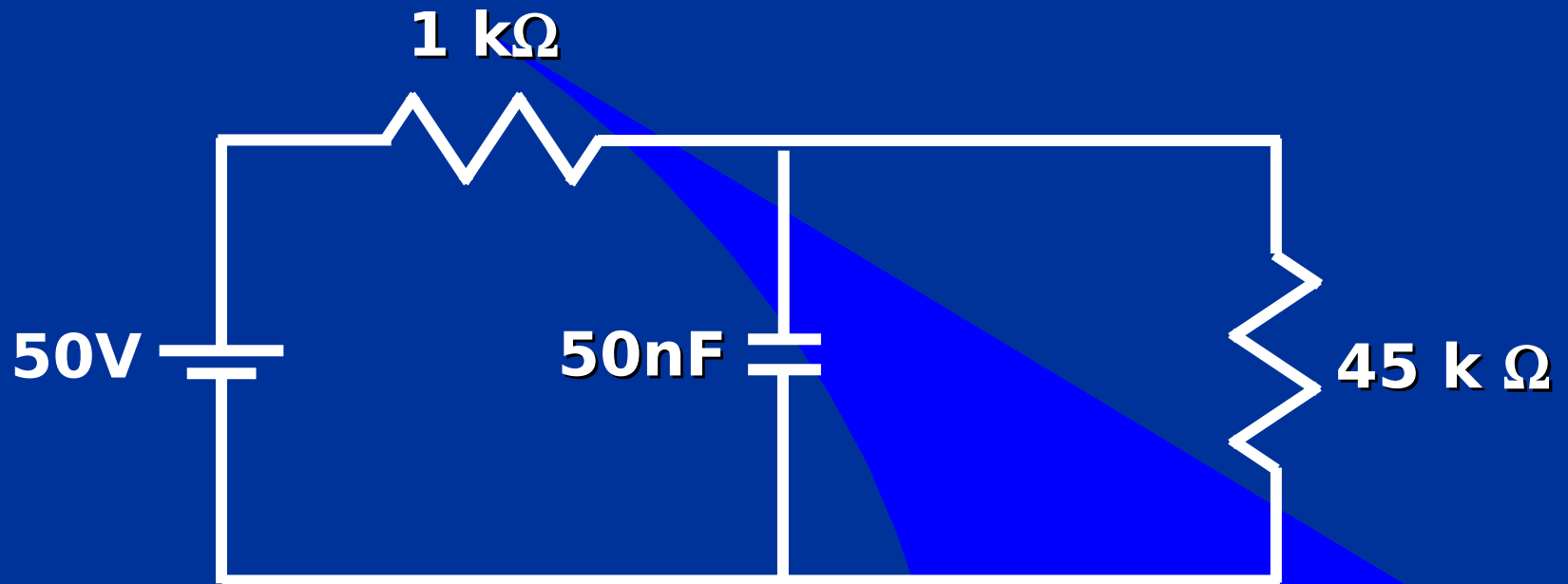




# Example 1 – 1st Order System

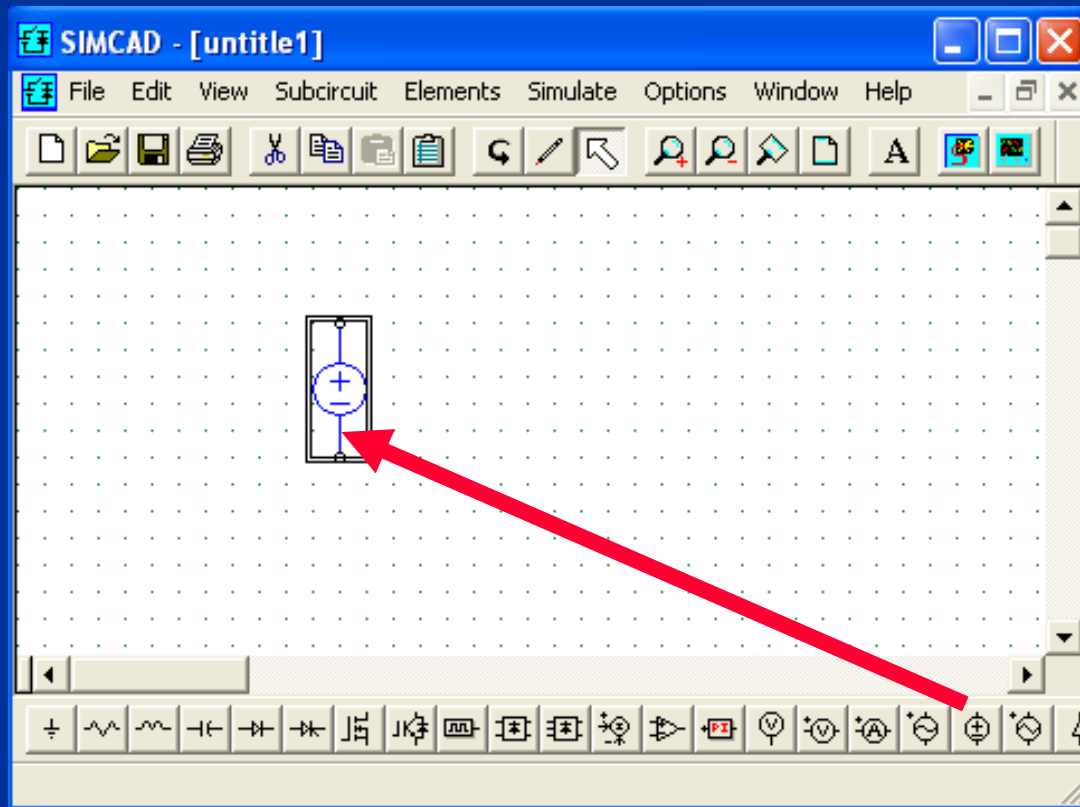**Insert a *DC Voltage Source* from the Element Toolbar.**




# Example 1 – 1st Order System

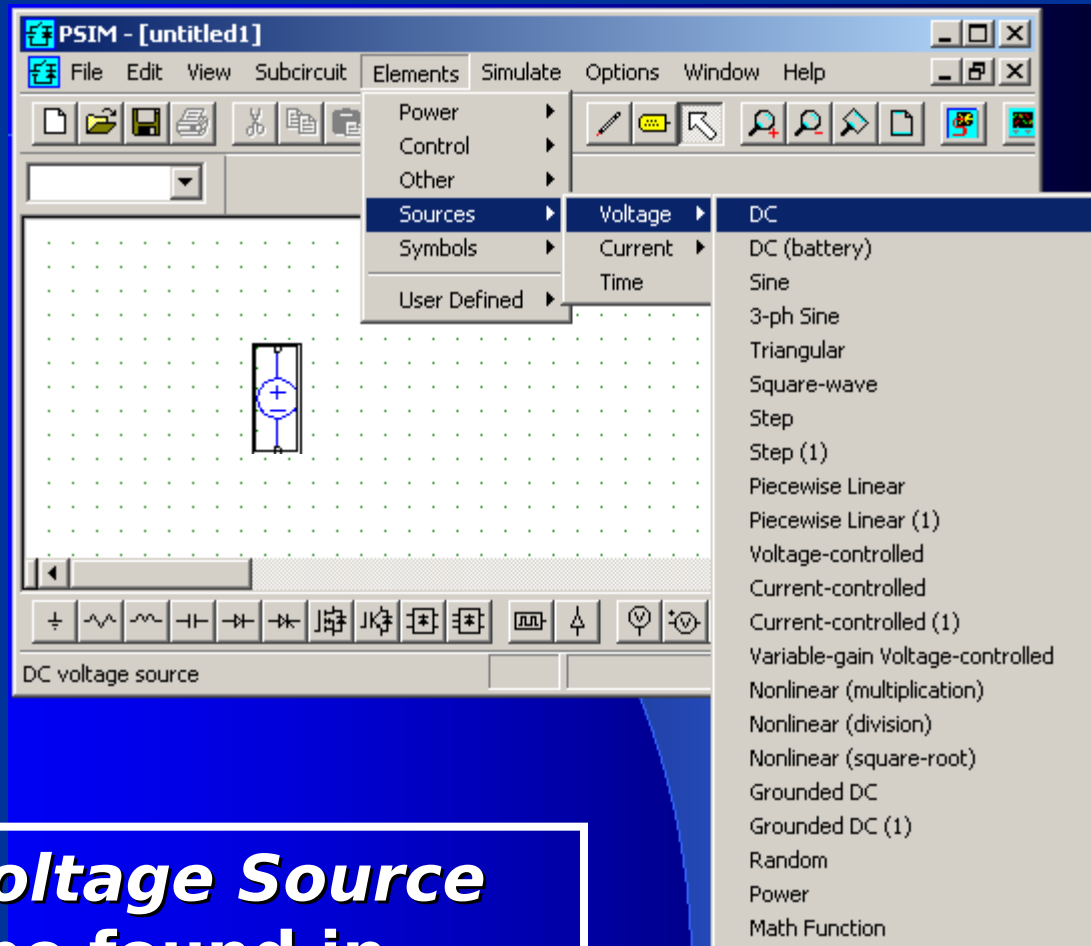

**The *DC Voltage Source* can also be found in *Elements > Sources > Voltage > DC***

# Example 1 – 1st Order System

Add two *Resistors* to the circuit.

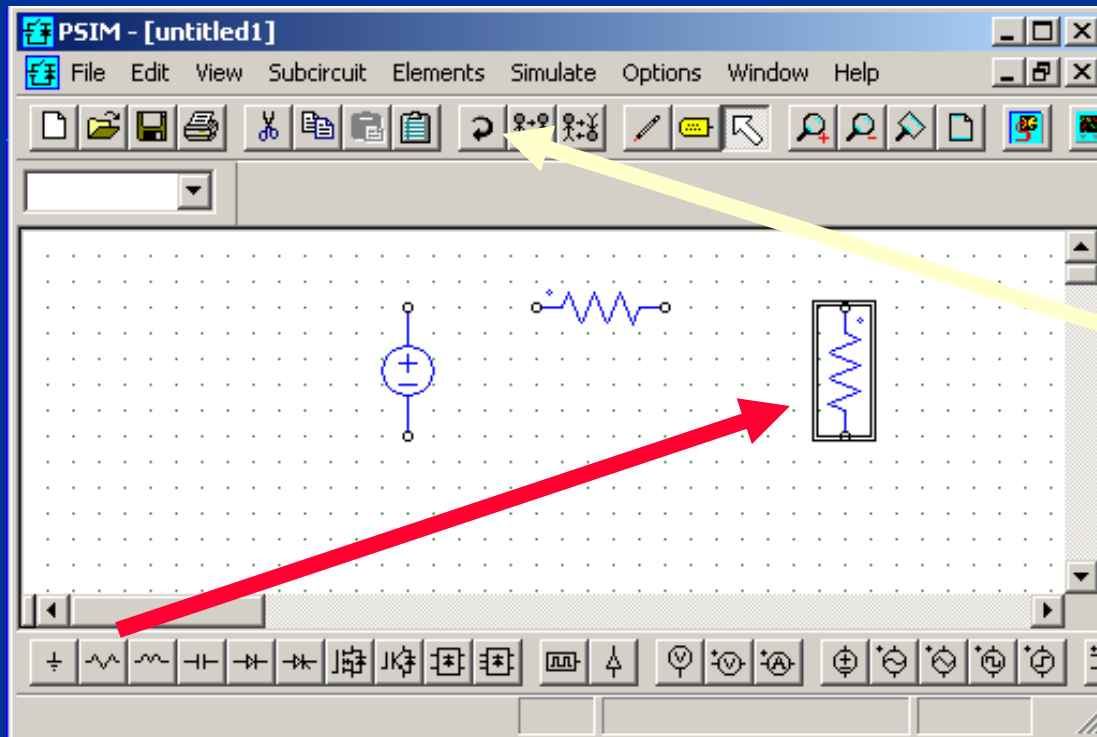


To rotate an element click with the right button...

... or use the icon *Rotate the Selection*.

# Example 1 – 1st Order System


**Add a *Capacitor* to the circuit.**

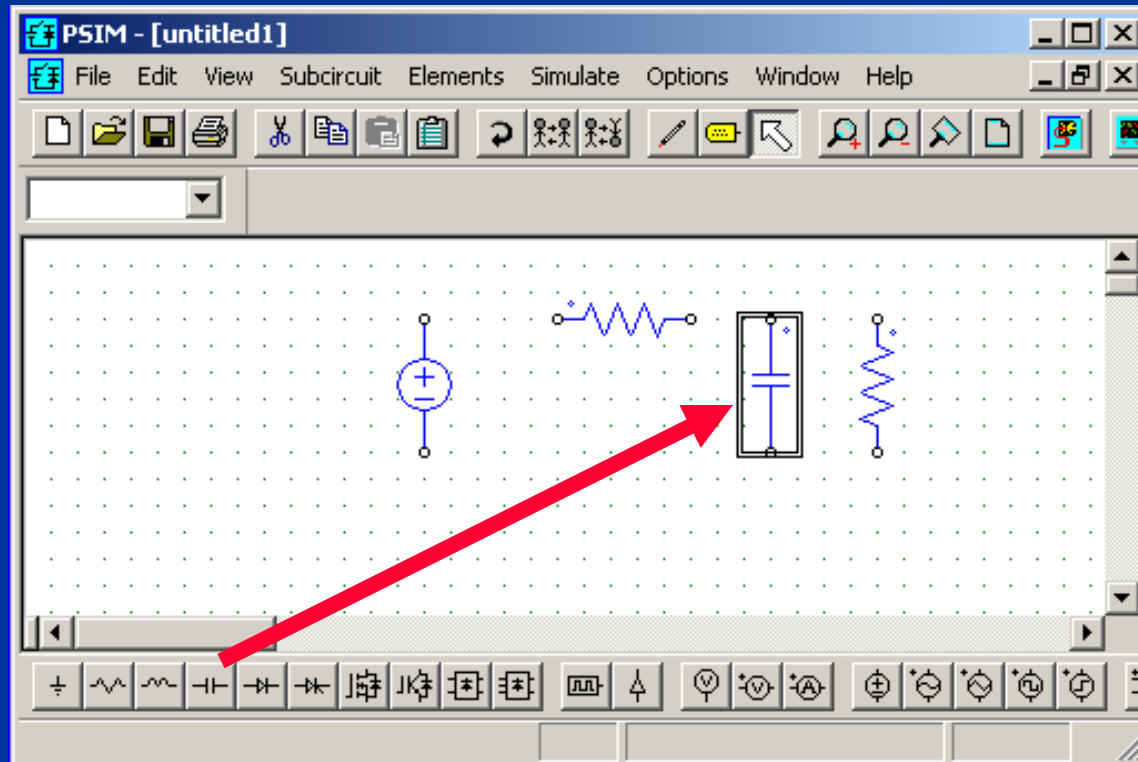
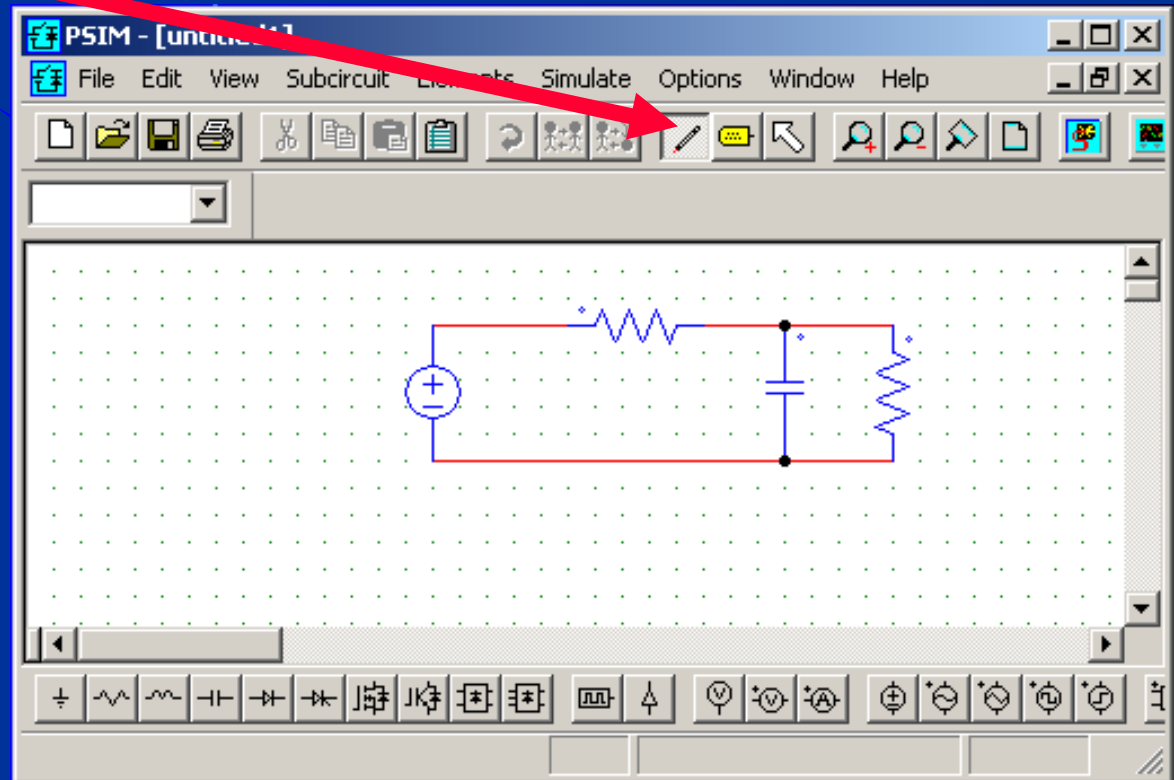
# Example 1 – 1st Order System


To connect the elements use the *Wire* tool.

Left-click on the circuit and drag the line with the mouse.




# Example 1 – 1st Order System

Insert a *Ground* element.

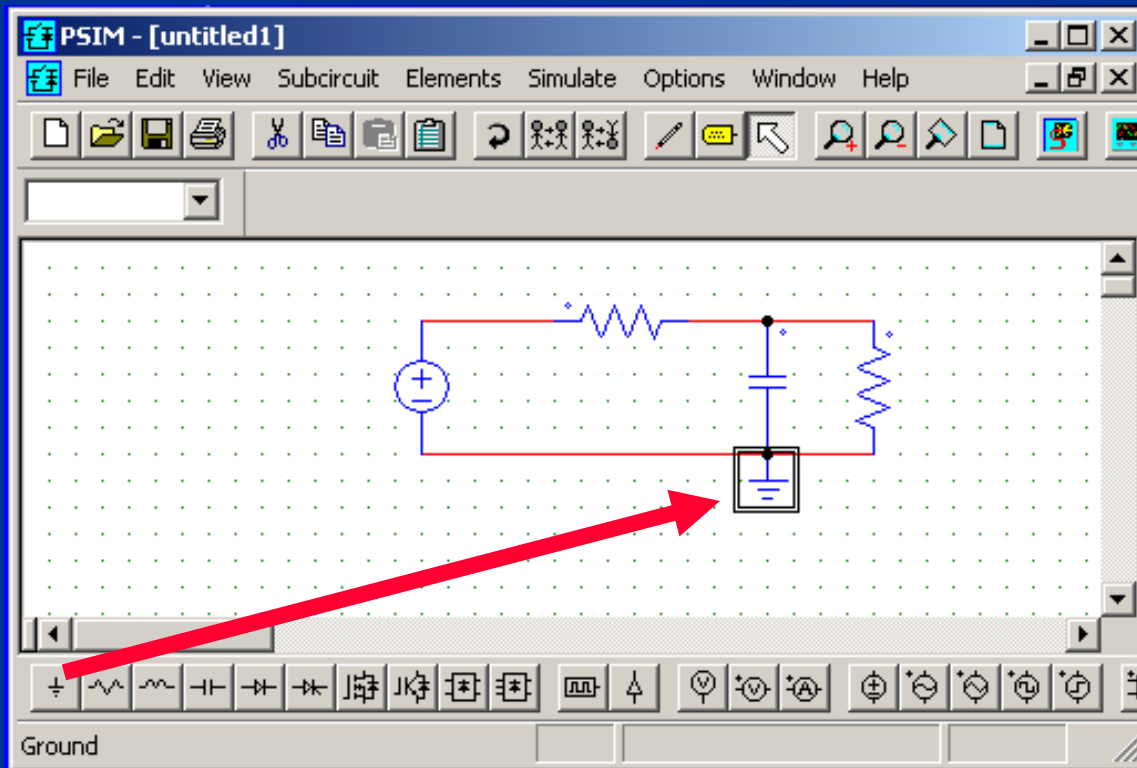

# Example 1 – 1st Order System

Set all the parameters values.

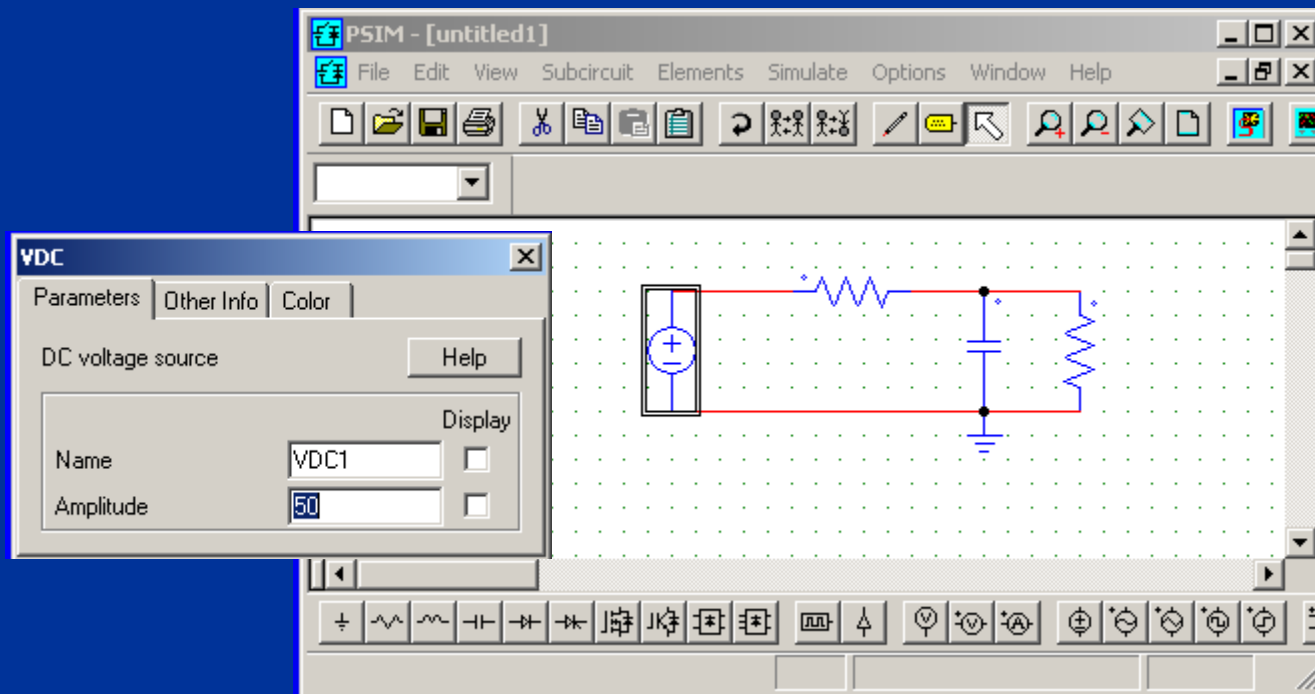


**Double-click on the element to set its parameters.**

**Just close the window to set the new value.**

# Example 1 – 1st Order System

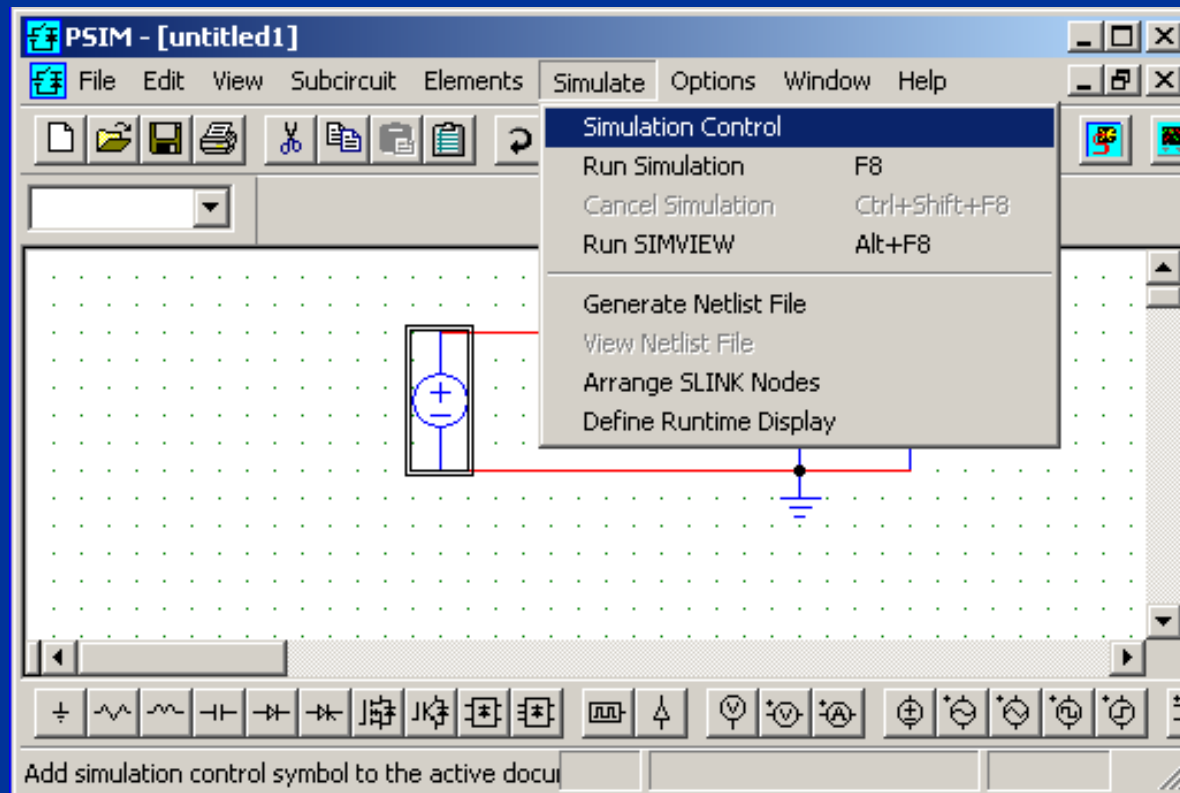
**Set the simulation parameters: Insert a *Simulation Control* block.**





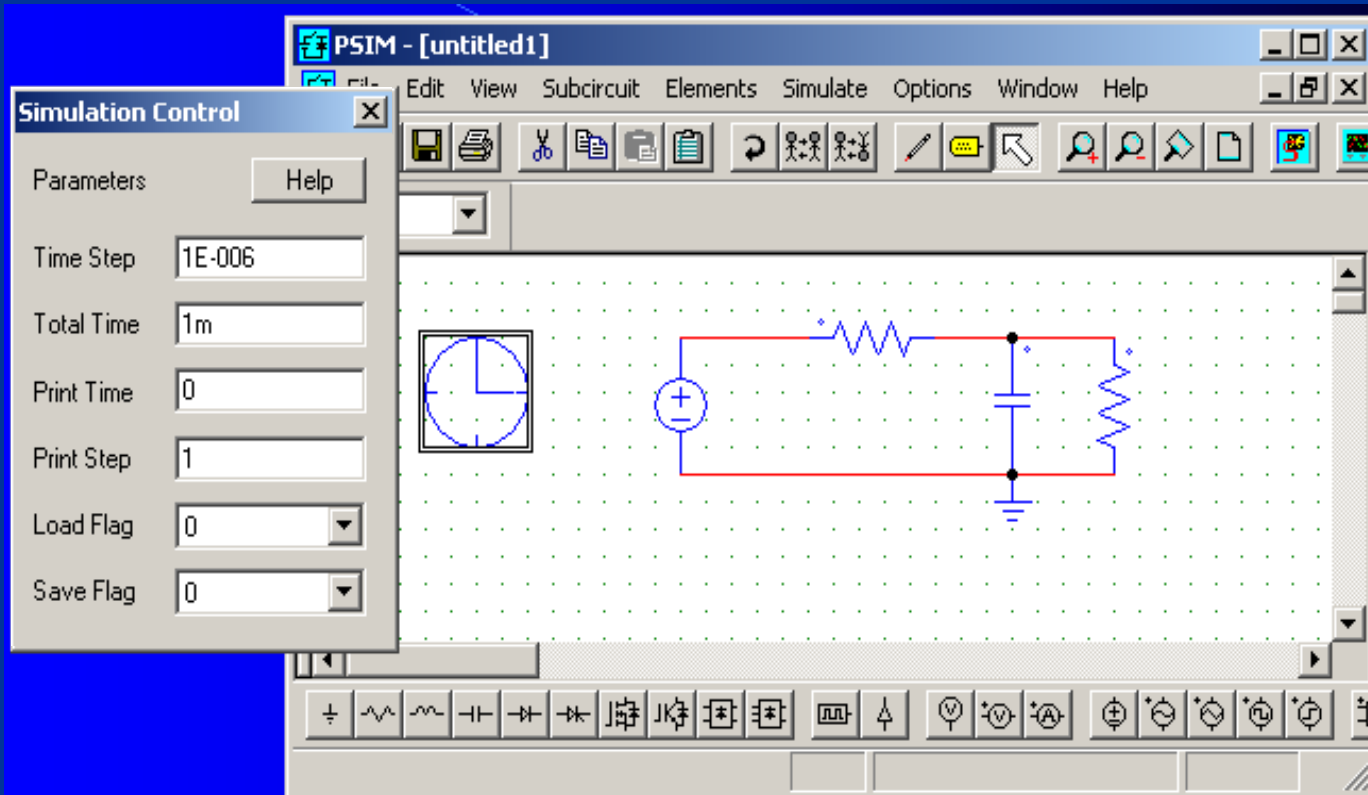
# Example 1 – 1st Order System

Set the simulation parameters: *Time Step* and *Total Time*.



# Example 1 – 1st Order System

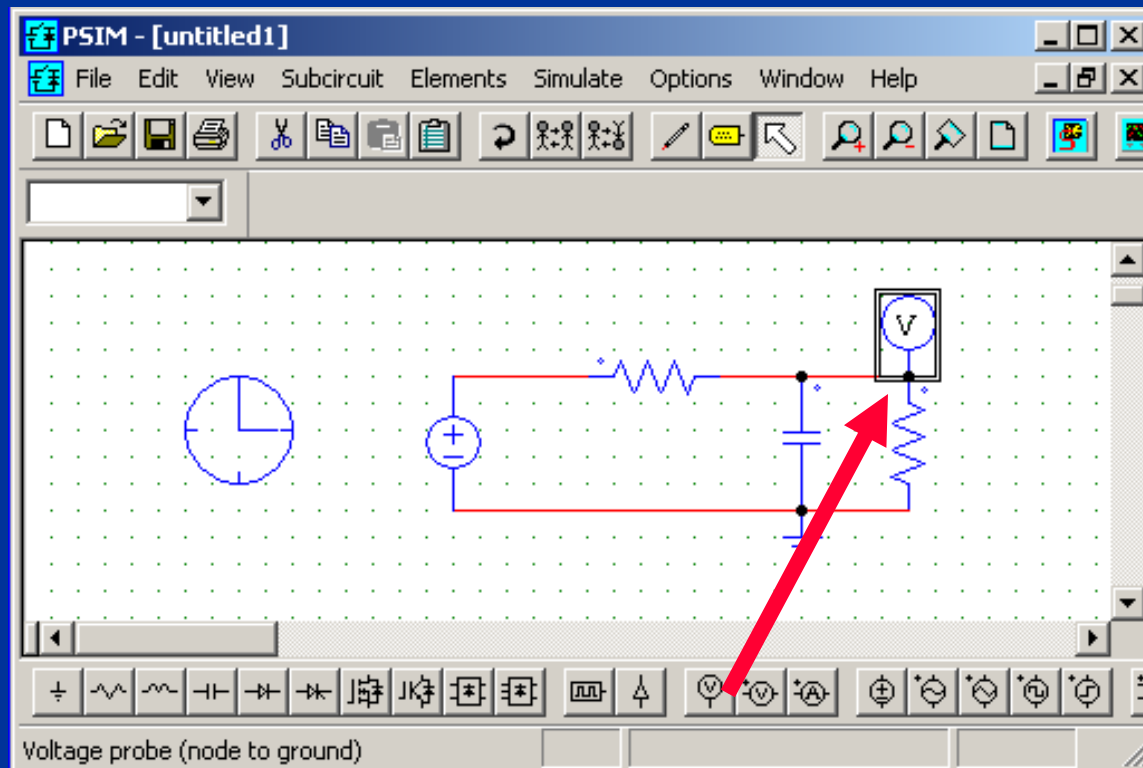
**Insert a *Voltage Probe* (node to ground).**




**Double-click on the voltage probe to change its name to  $V_o$ .**

# Example 1 – 1st Order System

**Start the simulation**

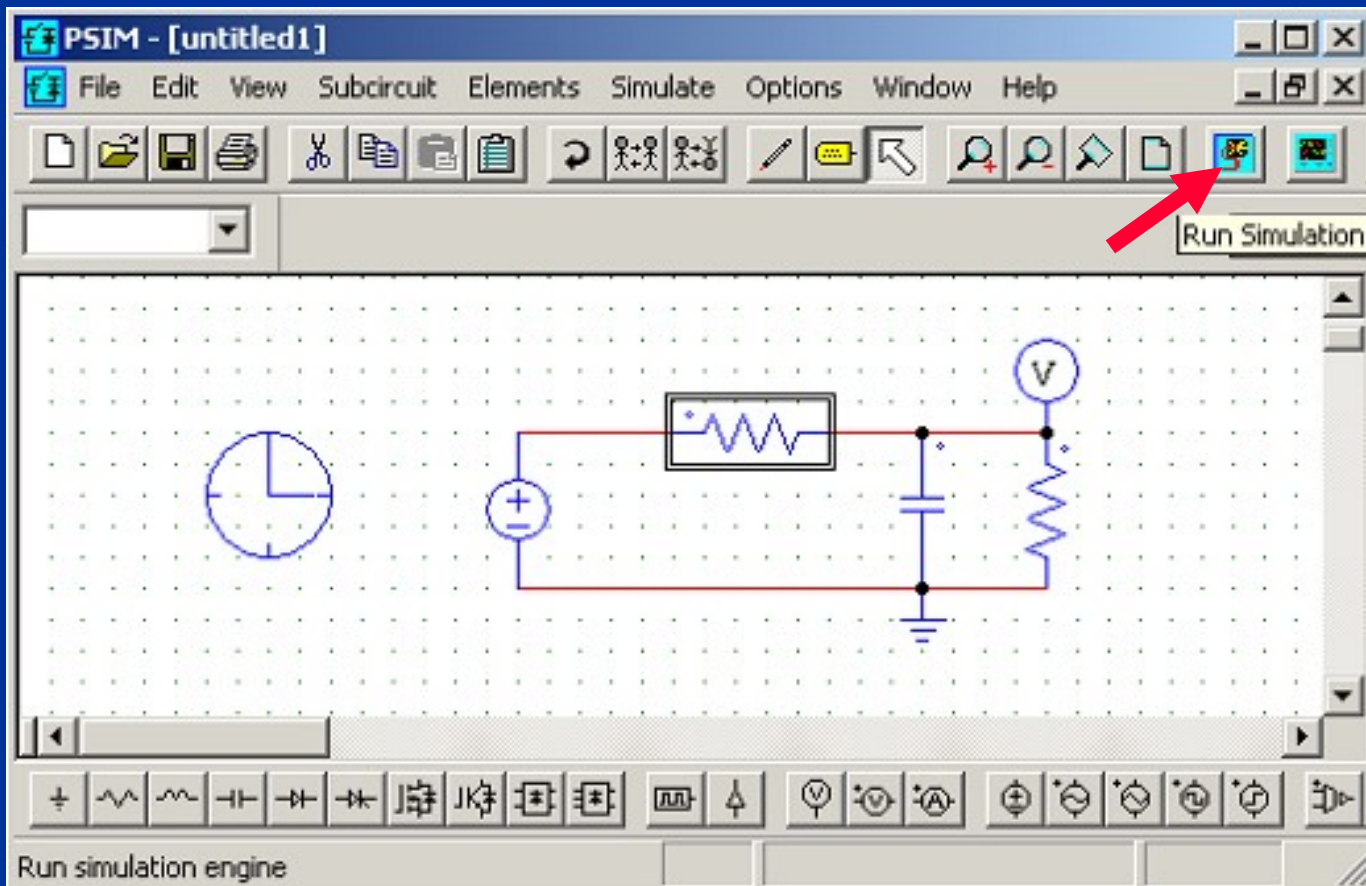


# Example 1 – 1st Order System

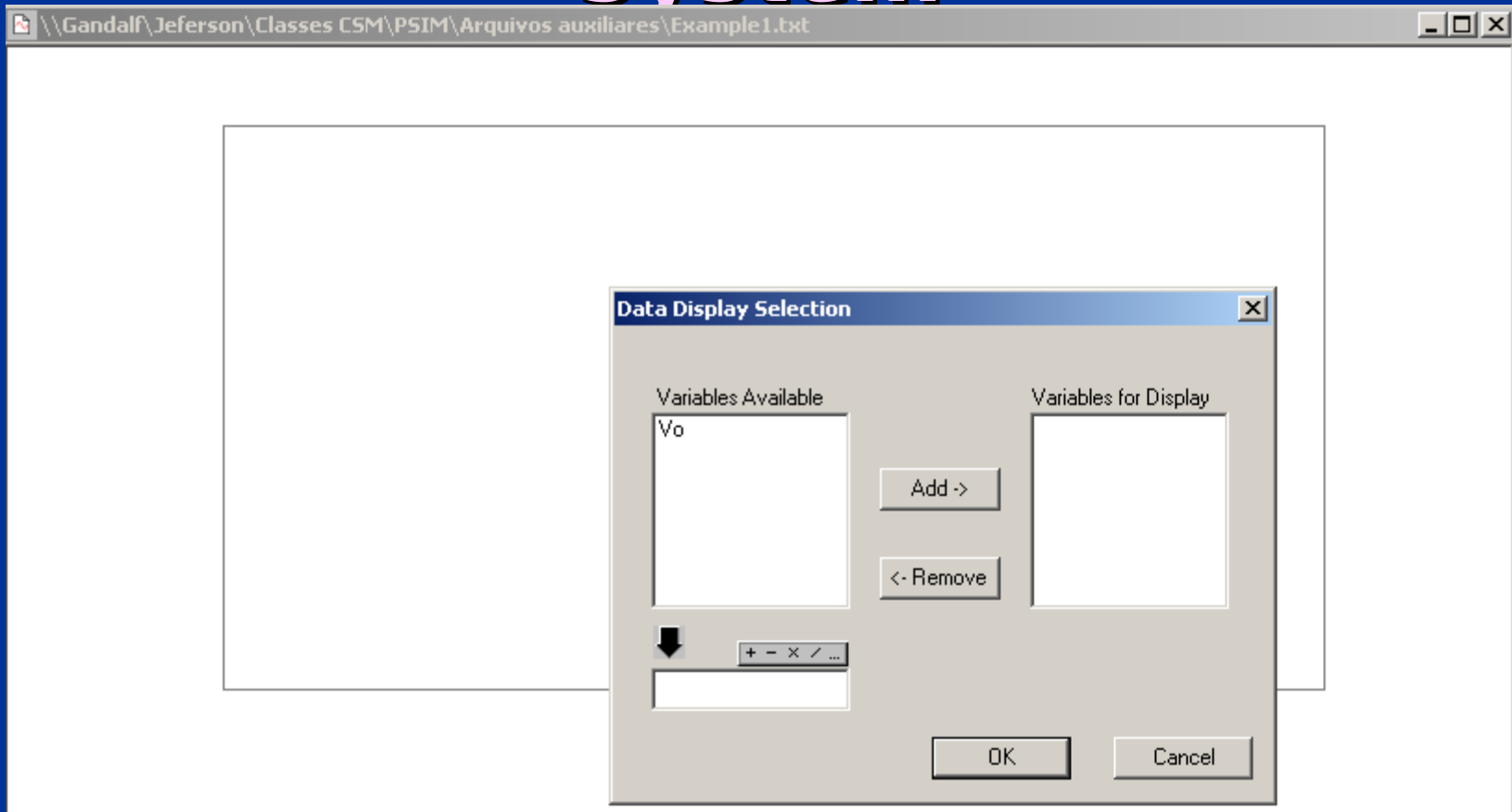

**Select the variable  $V_o$ .**


# Example 1 – 1st Order System

Set the colors.

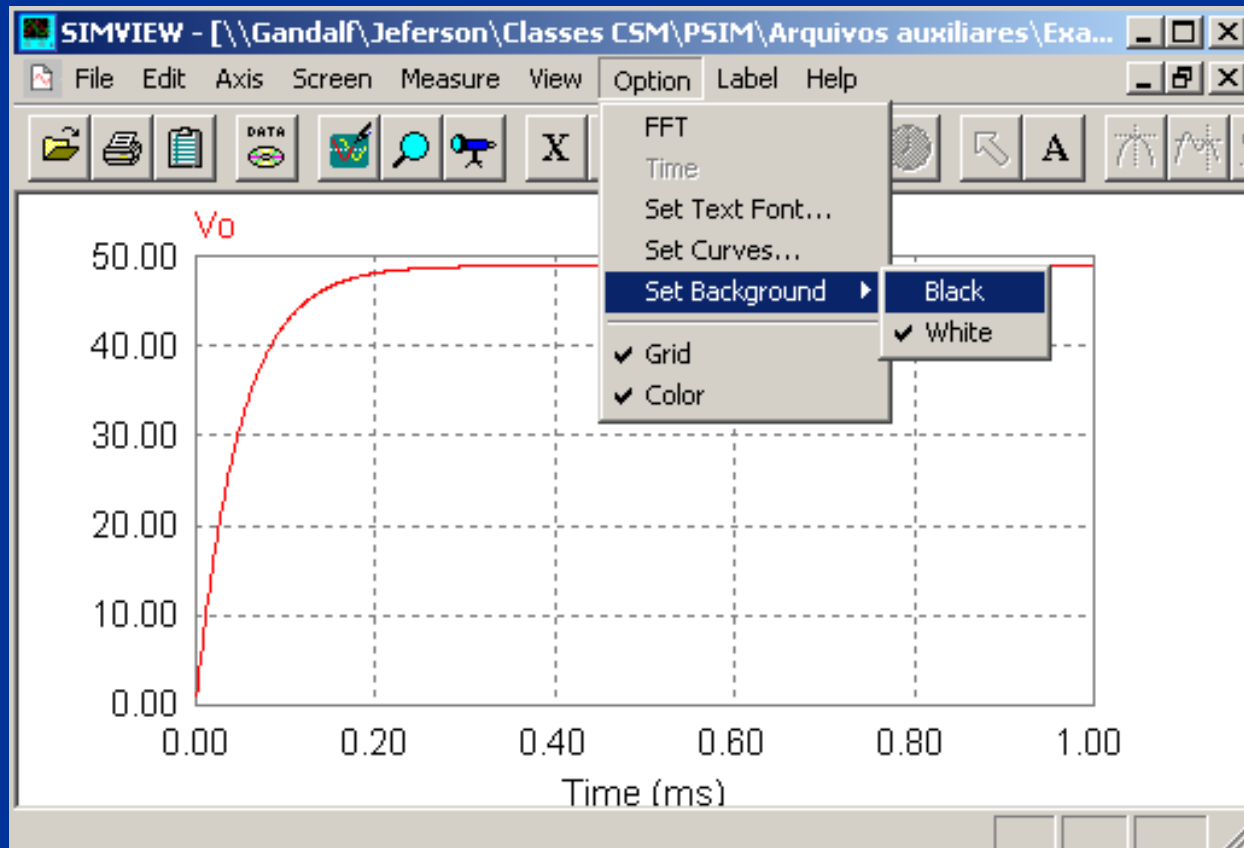

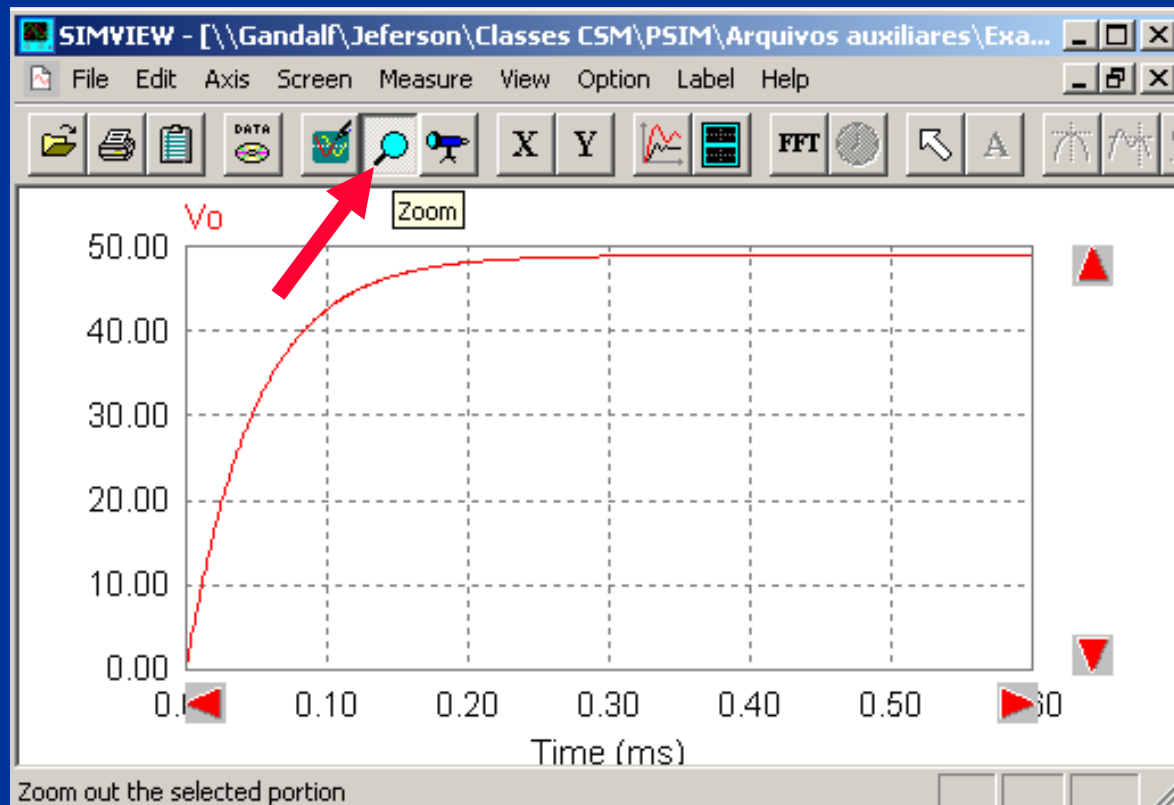
# Example 1 – 1st Order System

Use the *Zoom* tool and buttons to select a specific area you want to see.



# Example 1 – 1st Order System


Output file: \*.txt

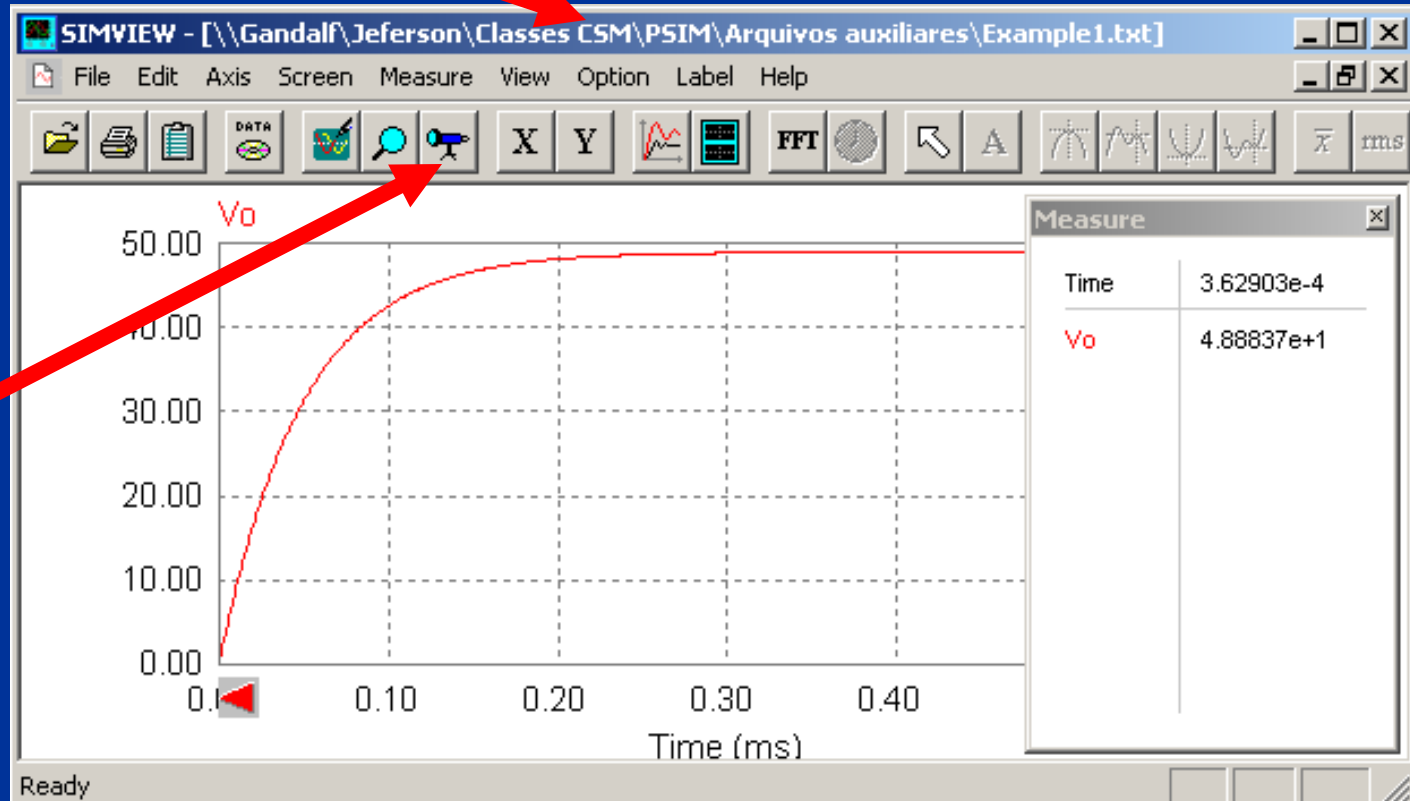

**Measure tool.**

**What is the expected steady-state output voltage?**


# Example 2: Voltage Controller

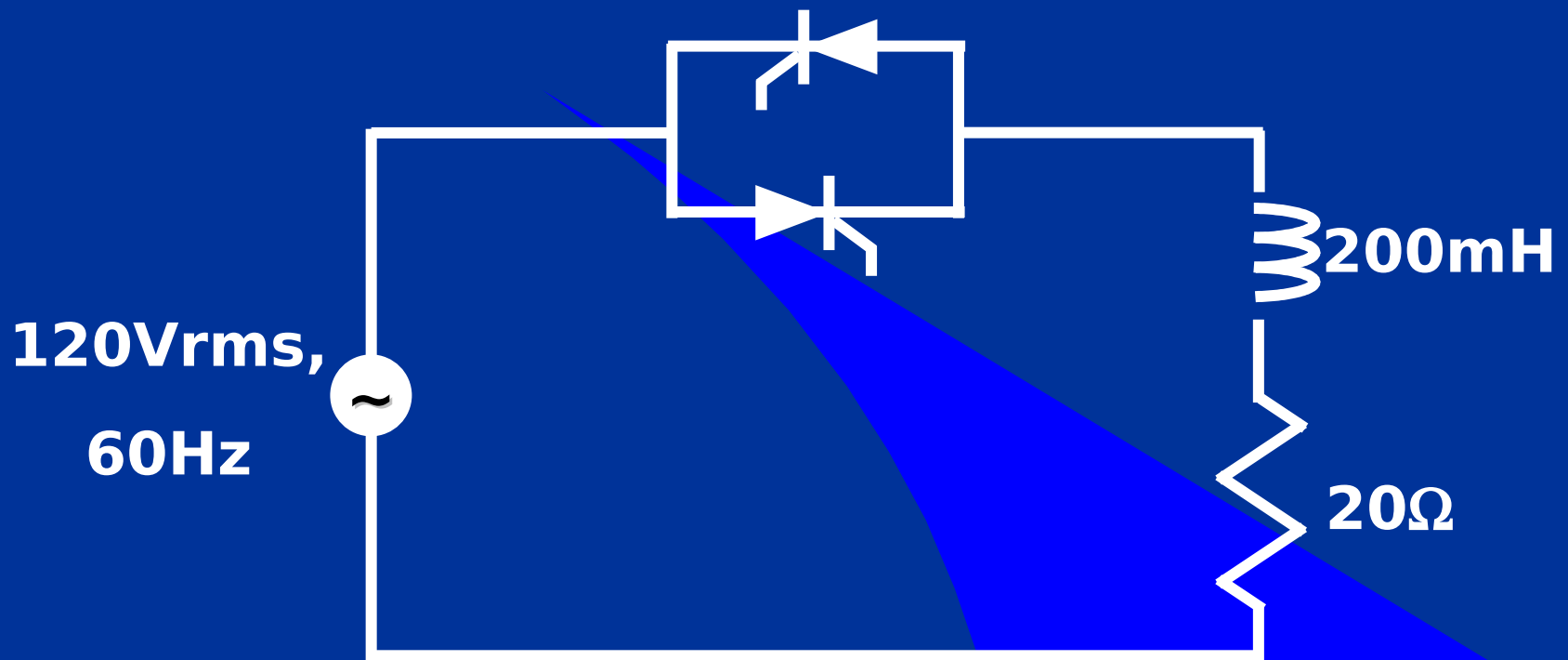




# Example 2: Voltage Controller

**Create a new circuit.**

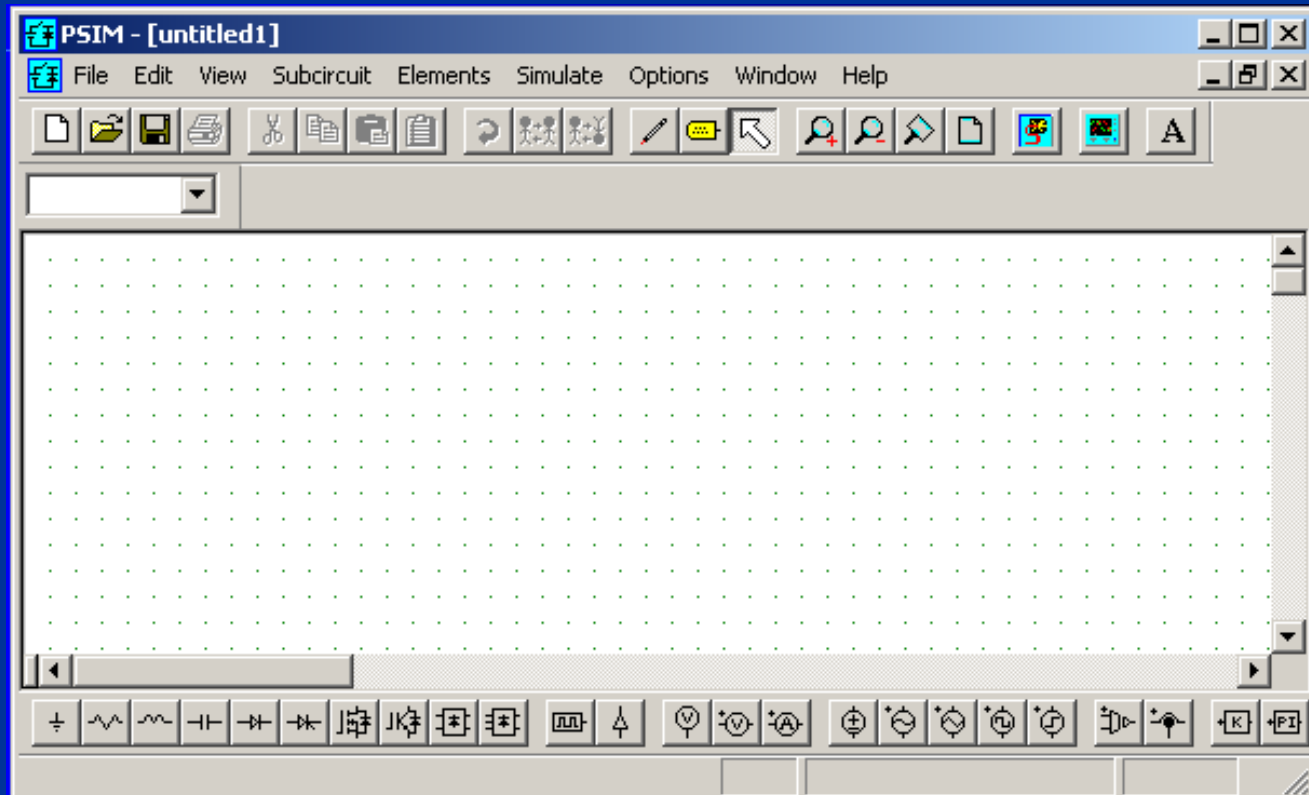


# Example 2: Voltage Controller

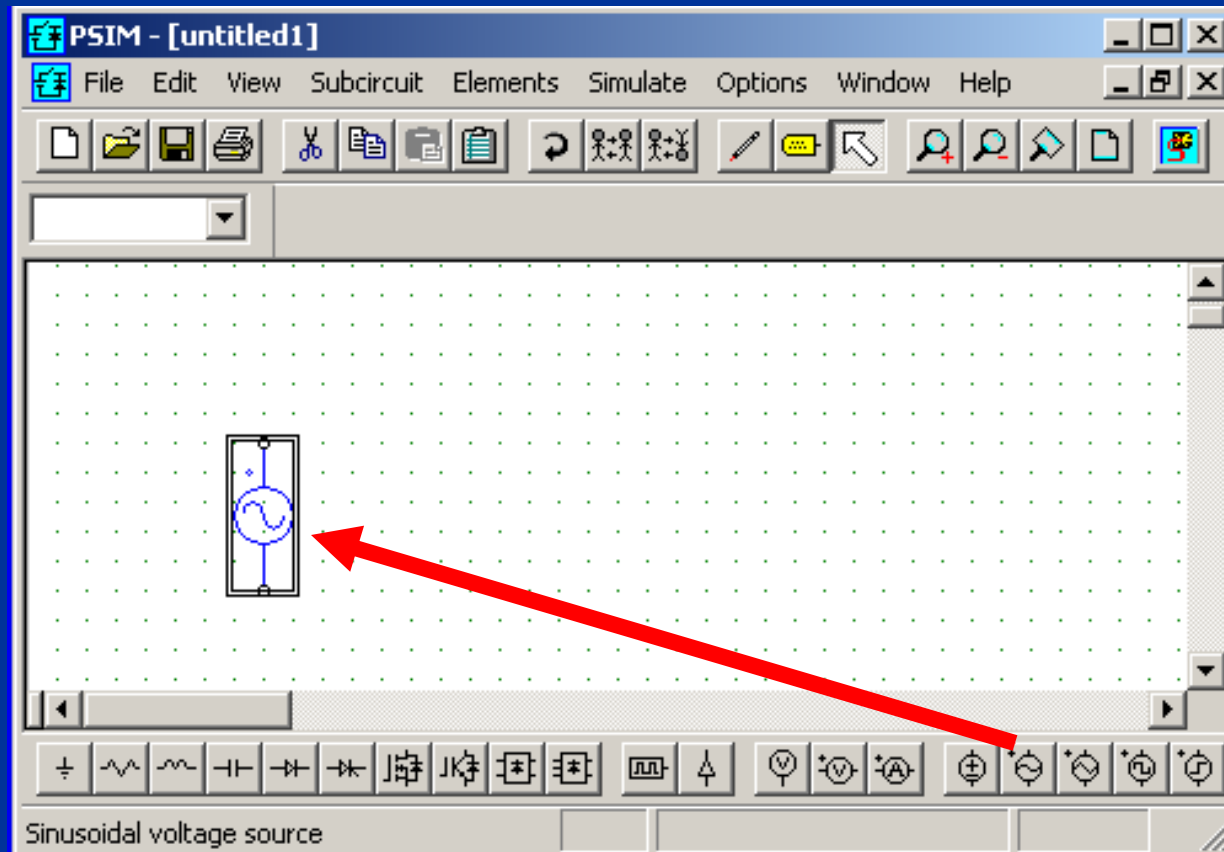**Insert a *Sinusoidal Voltage Source*.**




# Example 2: Voltage Controller

**Add two *Thyristors* to the circuit.**

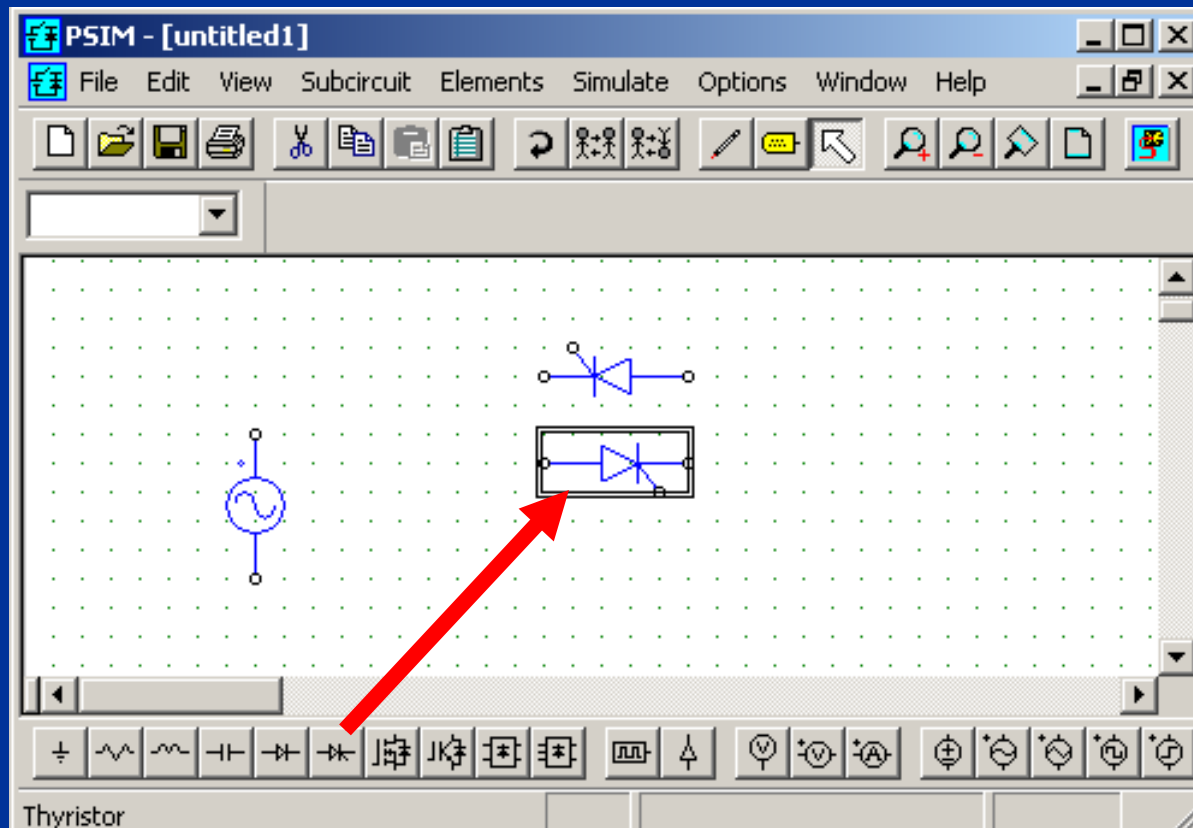


# Example 2: Voltage Controller

**Insert a *R-L Branch*.**

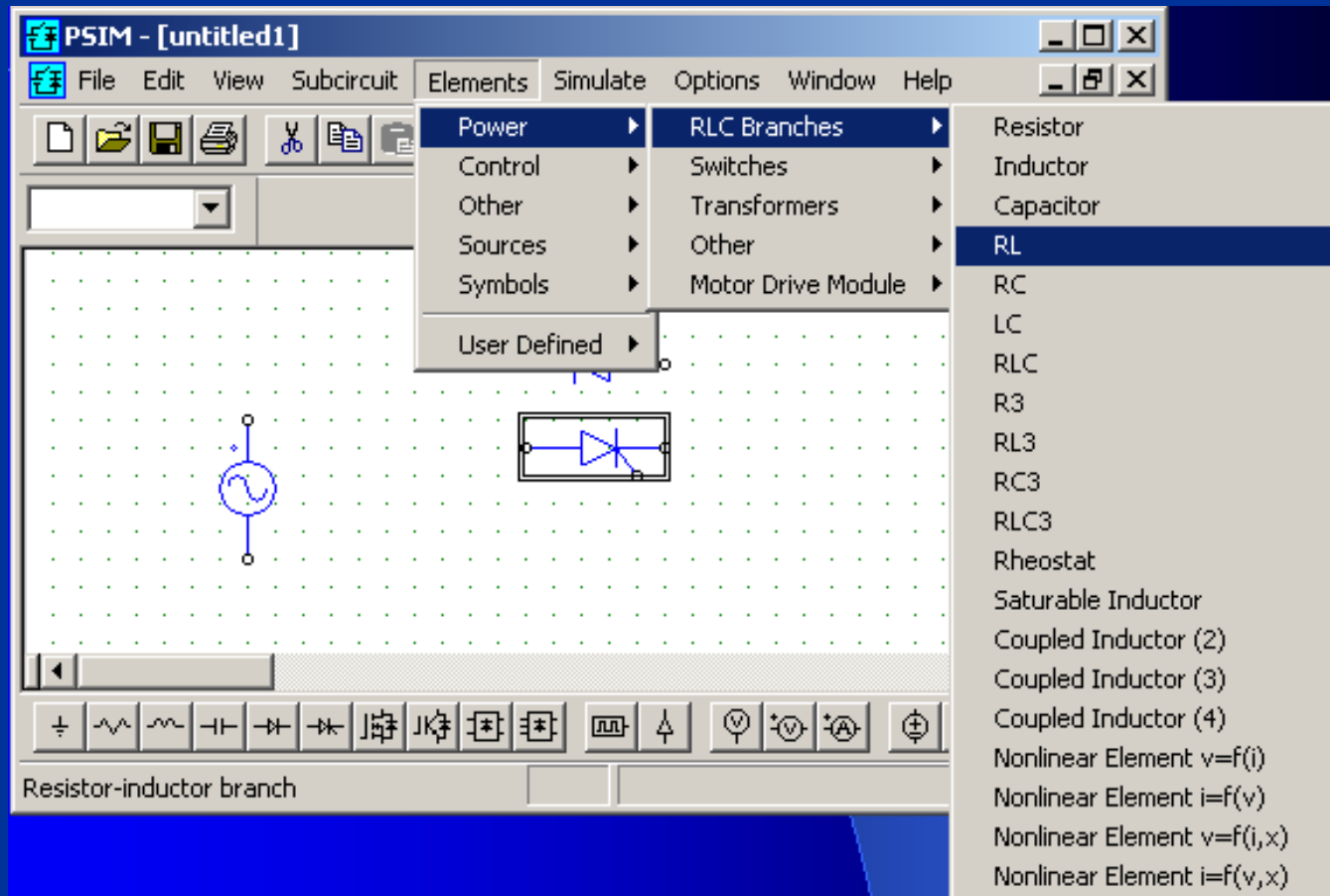


# Example 2: Voltage Controller

**Connect all the elements.**

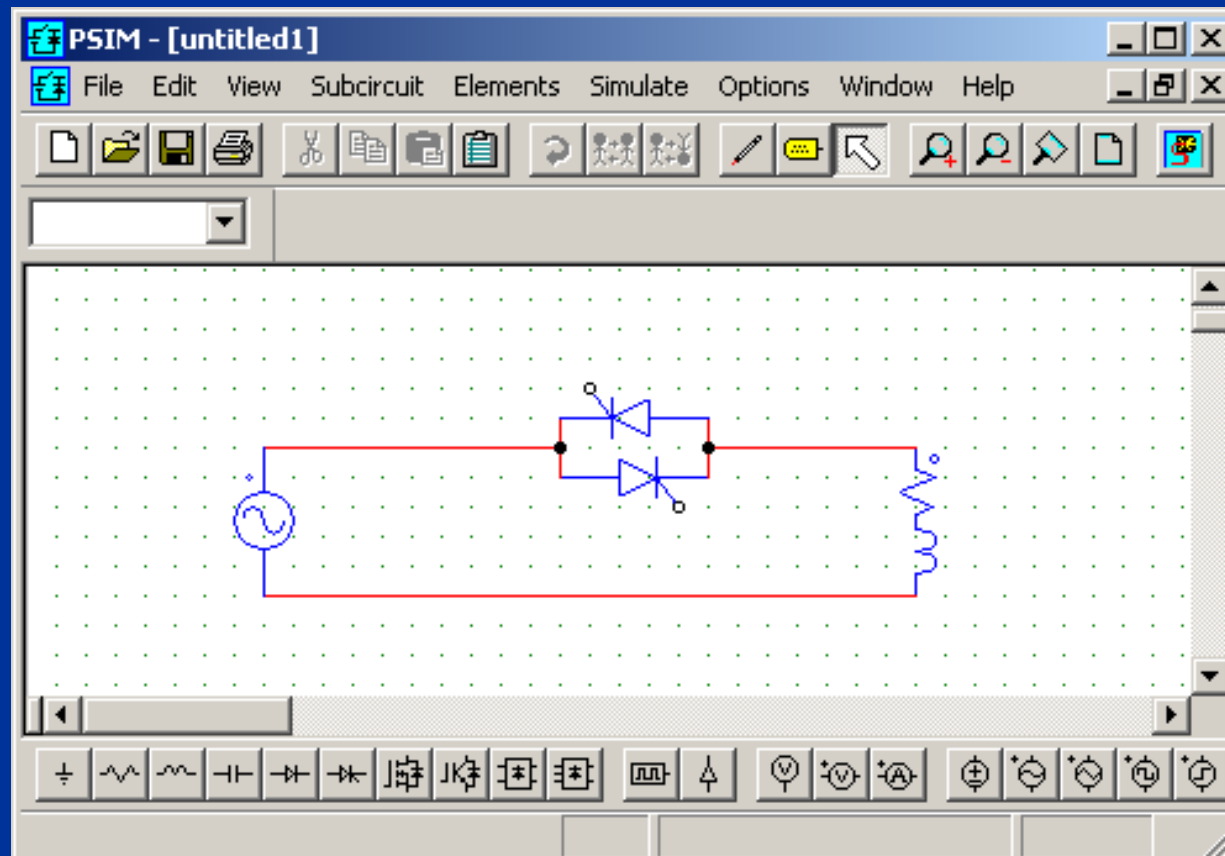


# Example 2: Voltage Controller

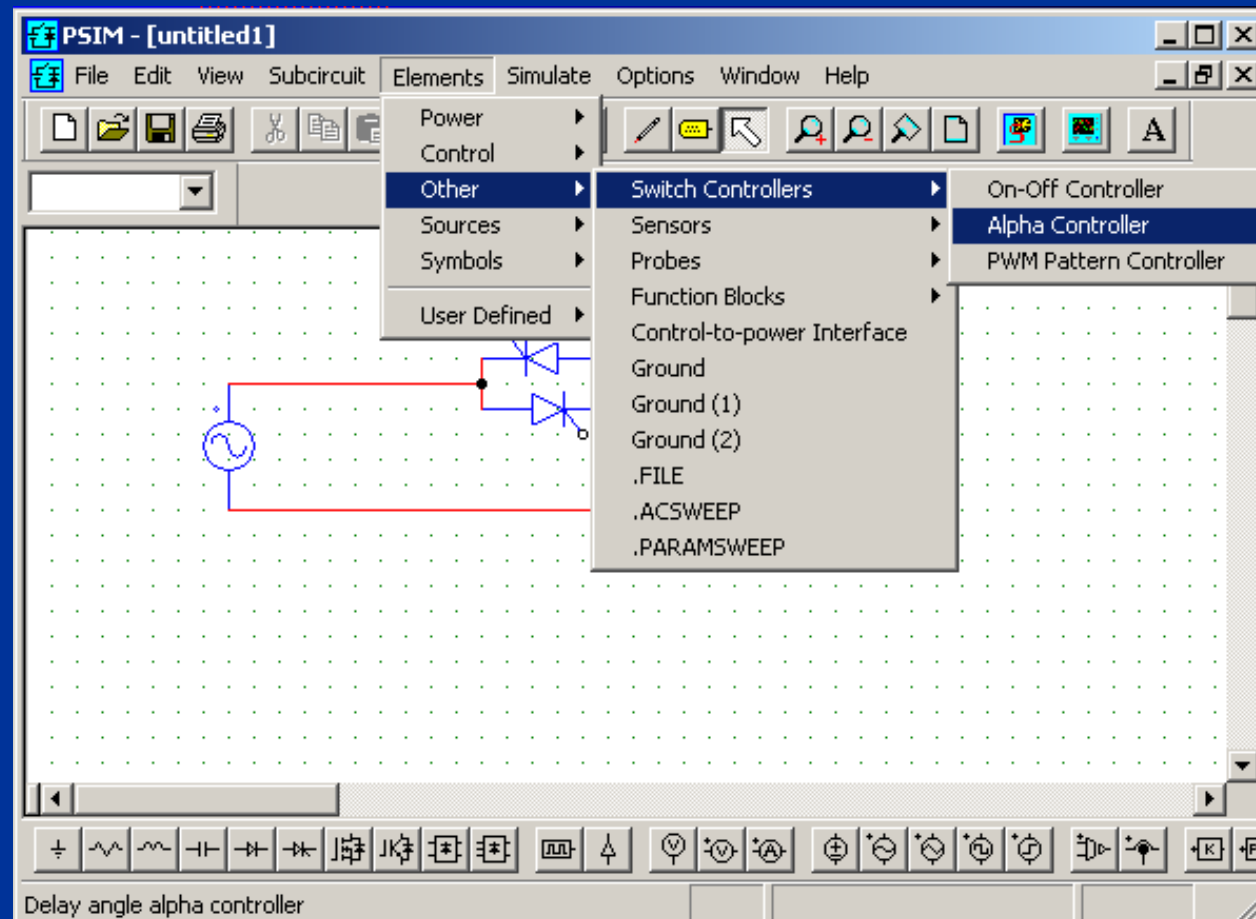**Add an *Alpha Controller* to the circuit.**




# Example 2: Voltage Controller

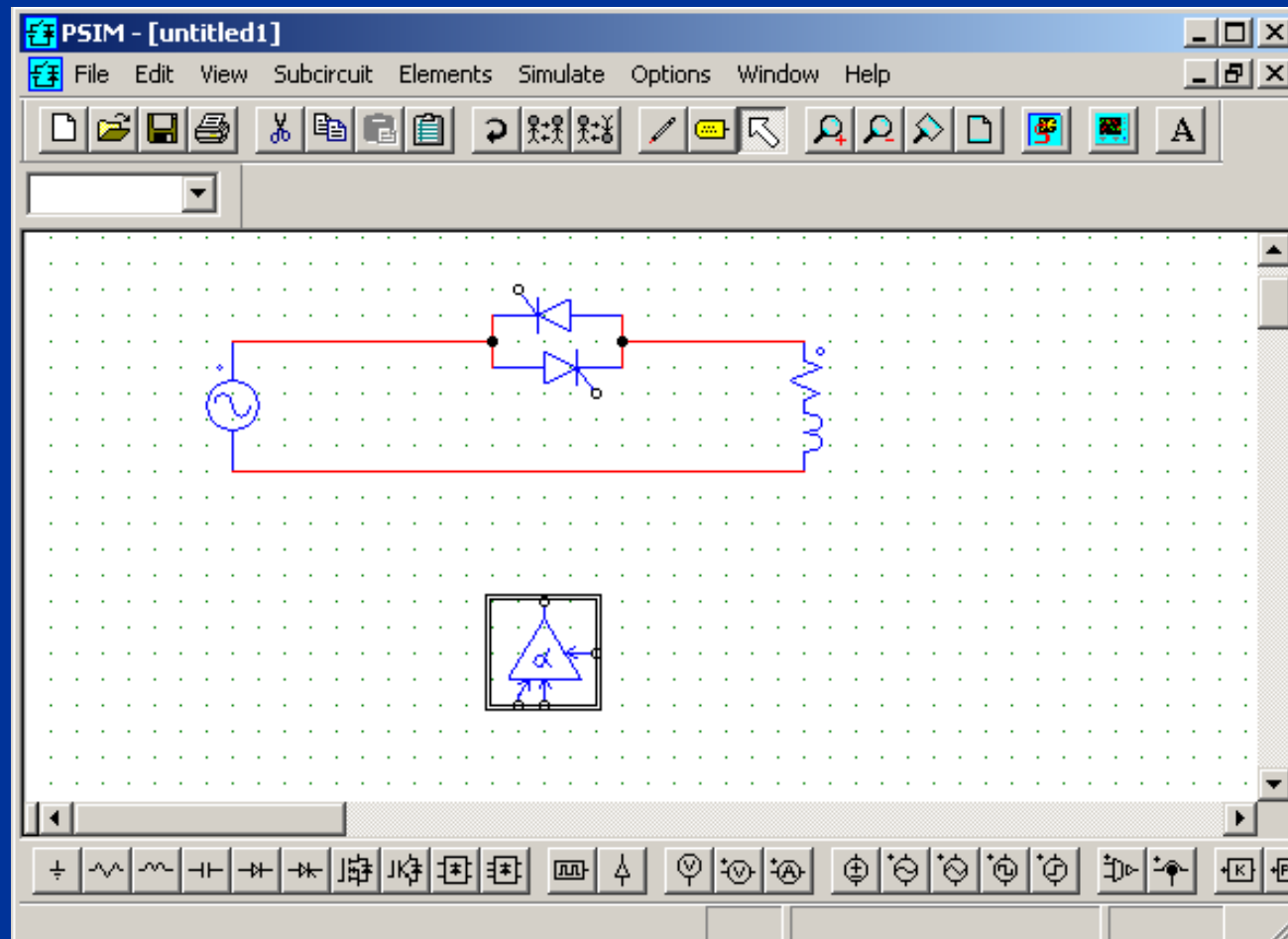

# Example 2: Voltage Controller

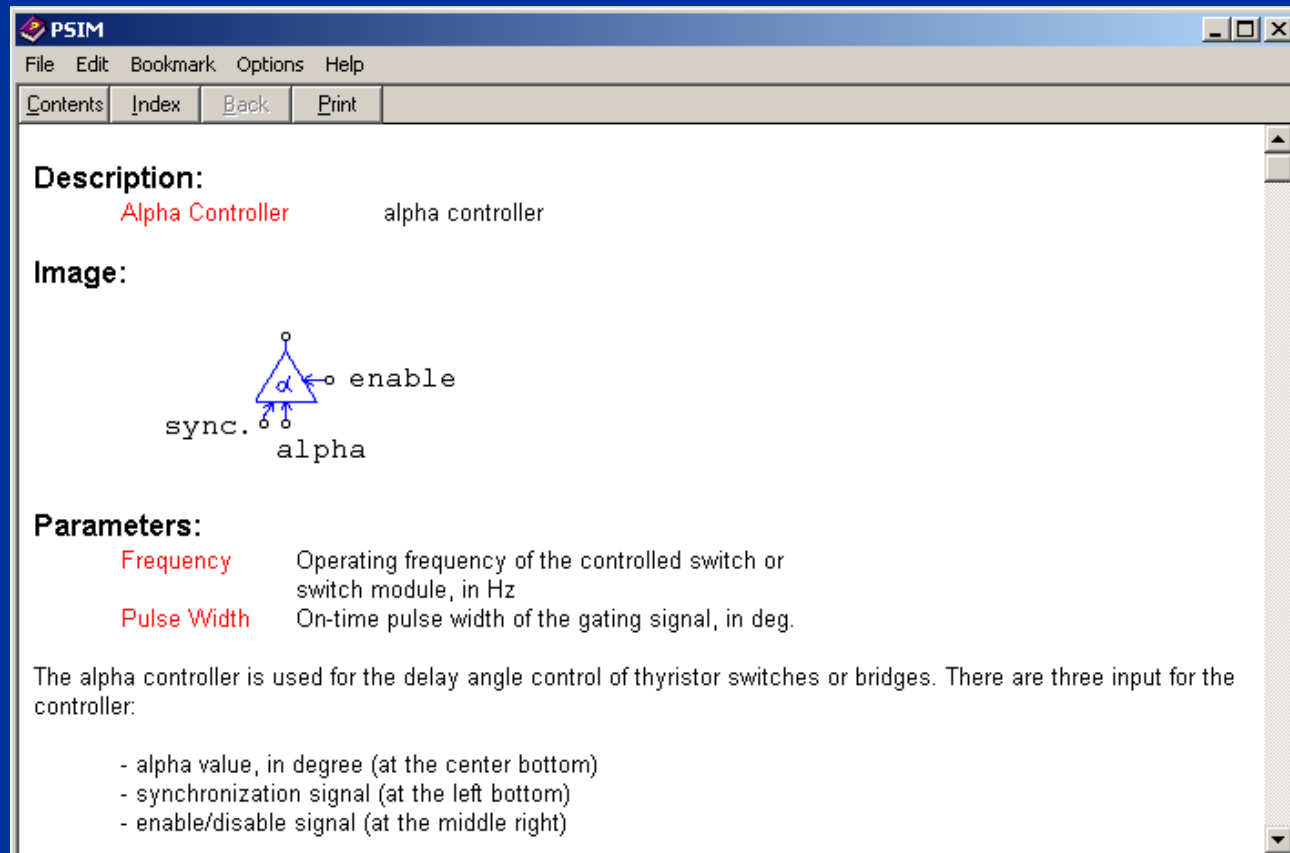
**Double-click on the block and click on *Help* to understand this block.**






# Example 2: Voltage Controller

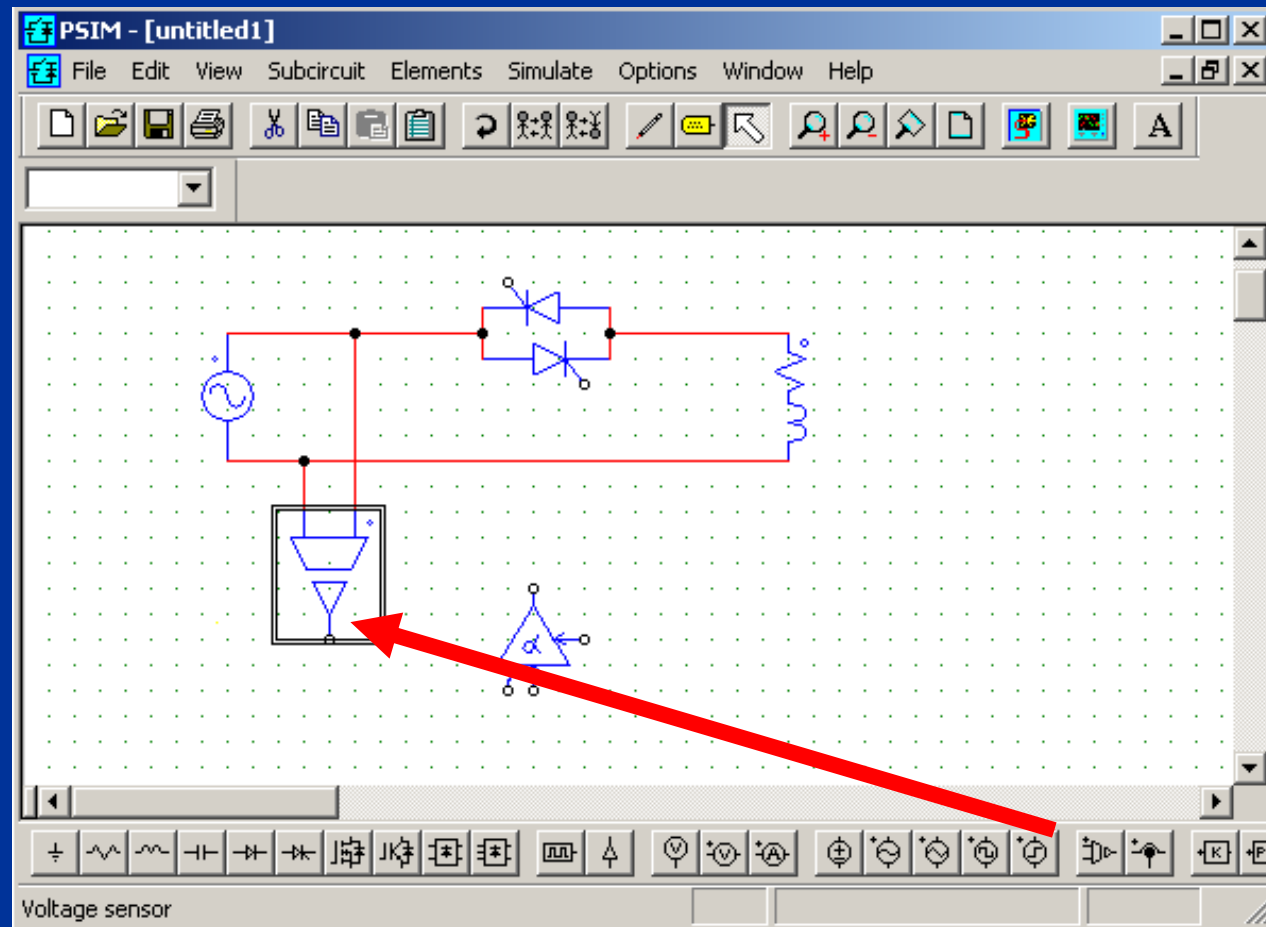**Add a *Voltage Sensor* to the circuit to synchronize the gating signal.**



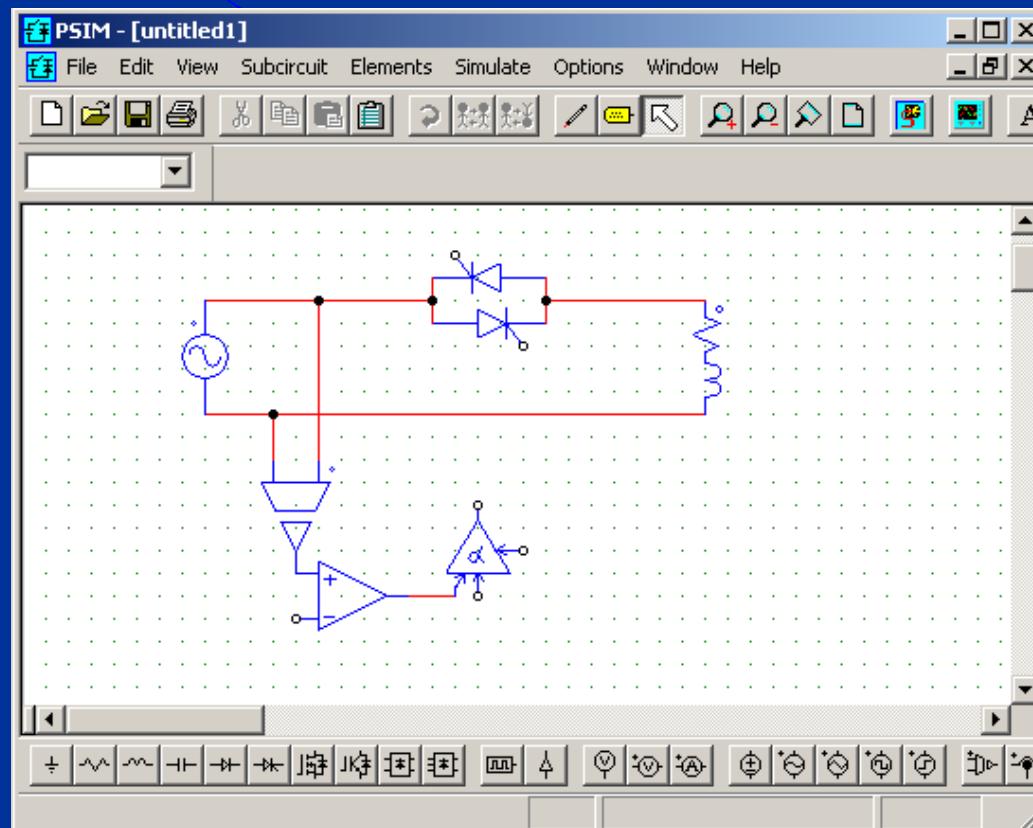
# Example 2: Voltage Controller

Insert a *Comparator* to detect the zero crossing  
(from *Elements > Control > Comparator* or  
from the Element toolbar)




# Example 2: Voltage Controller

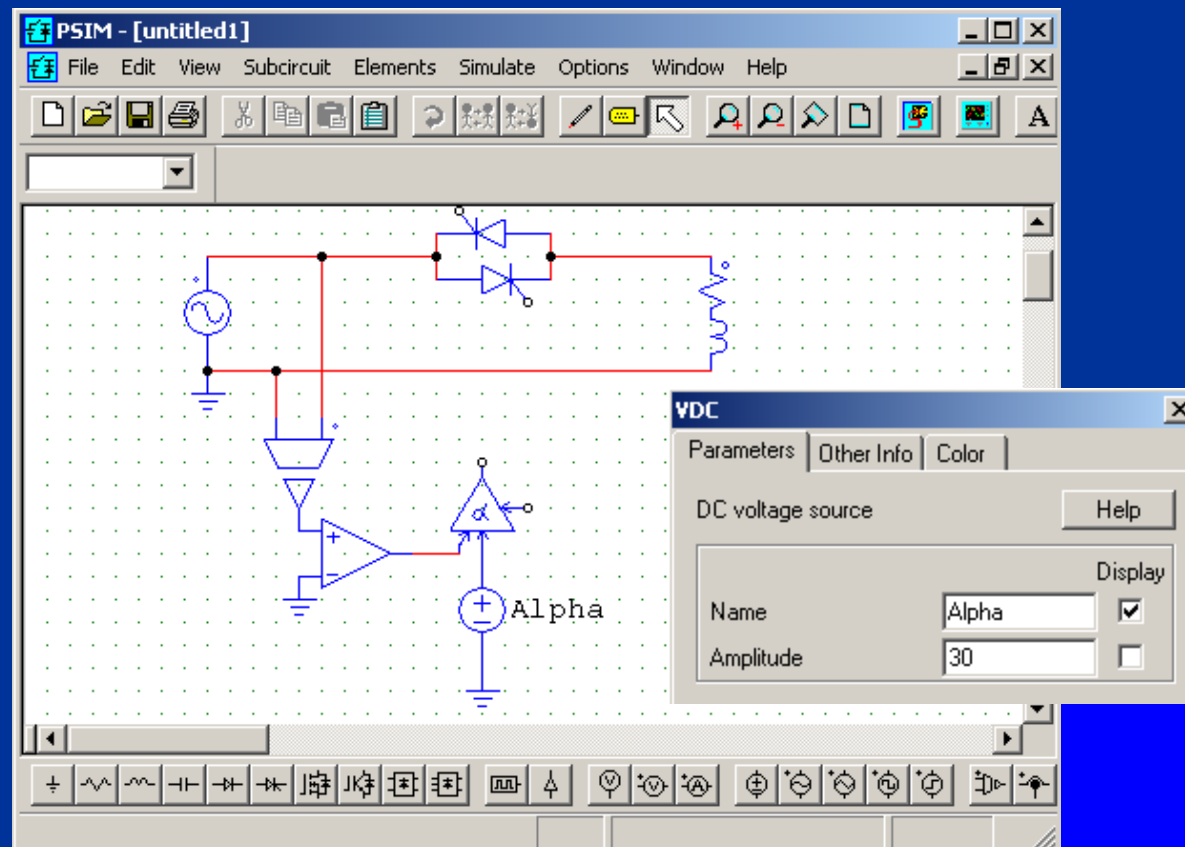**Add a *Ground* to the circuit. Insert a *DC Voltage Source*. Change its name to *Alpha* and display it.**



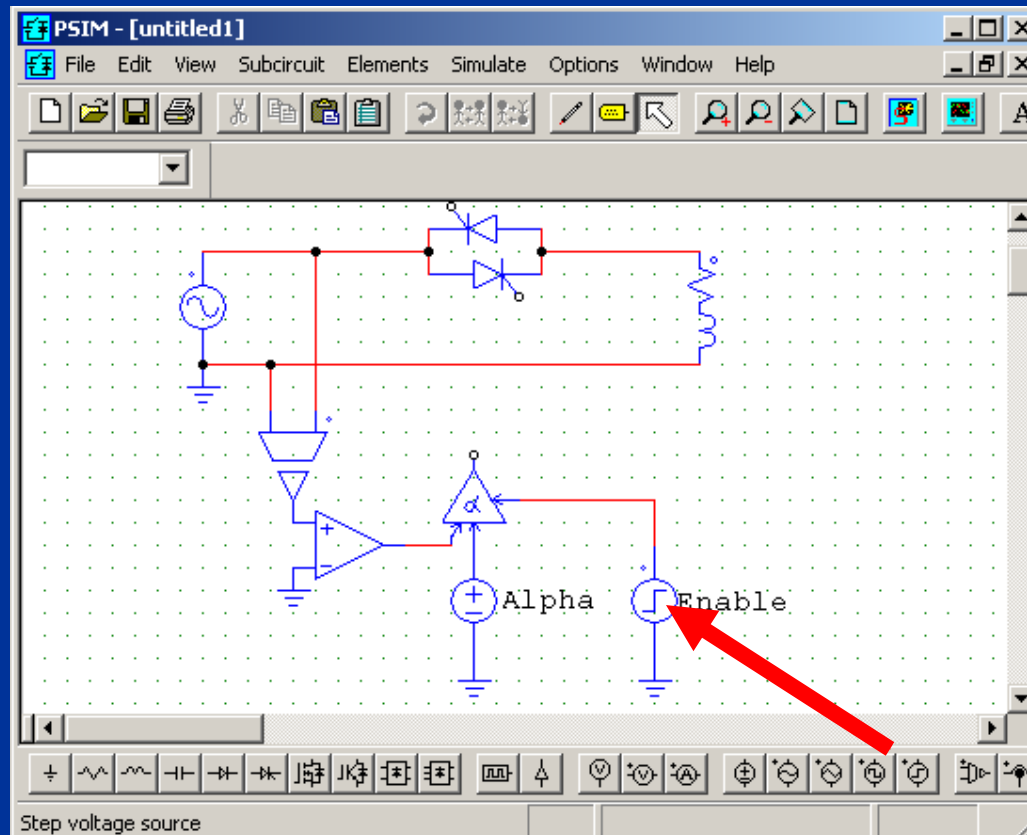
# Example 2: Voltage Controller

Insert a *Step Voltage Source*. Change its name to *Enable* and display it.



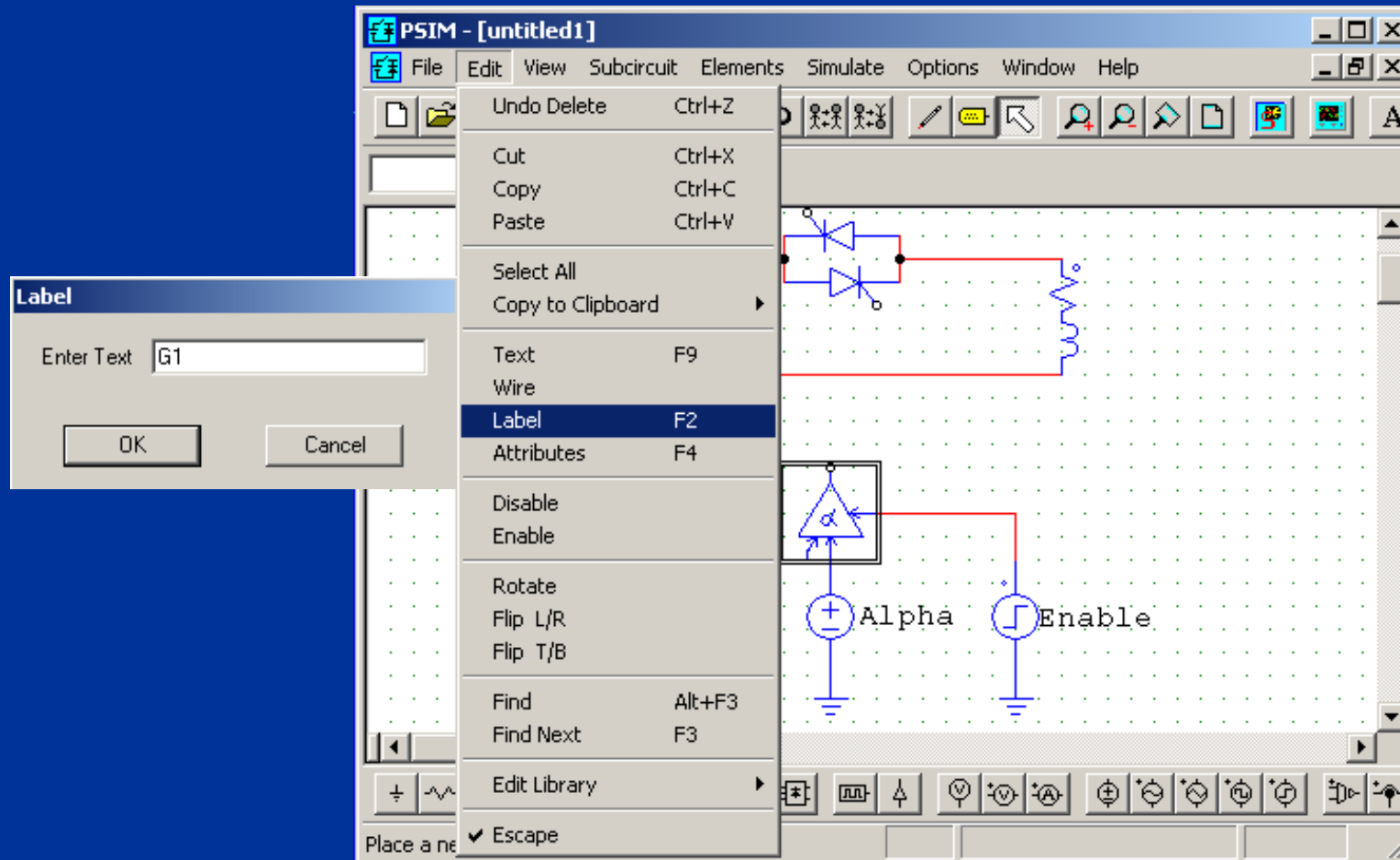
# Example 2: Voltage Controller

Using *Labels* to make connections: insert a *Label* and name it *G1*.


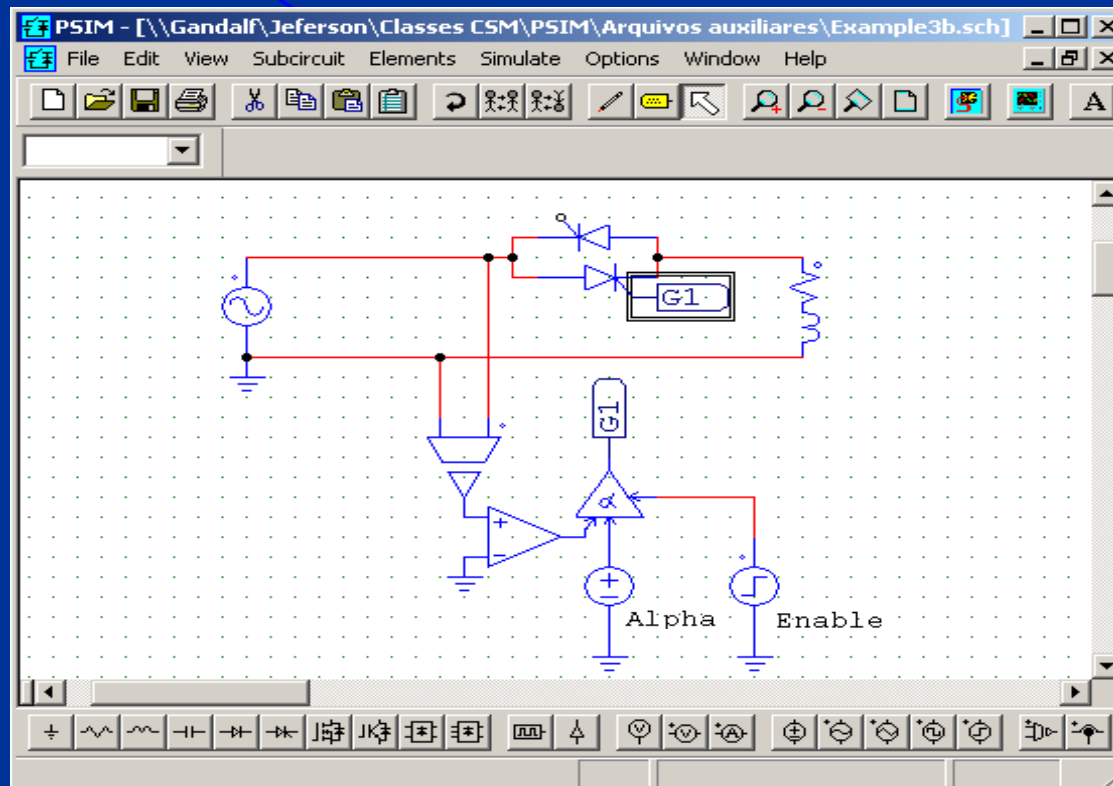
# Example 2: Voltage Controller


Connect the *Label* to the output of the *Alpha Controller* block. Insert another *Label*, name it *G1* and connect it to the gate port of *Thyristor 1*.


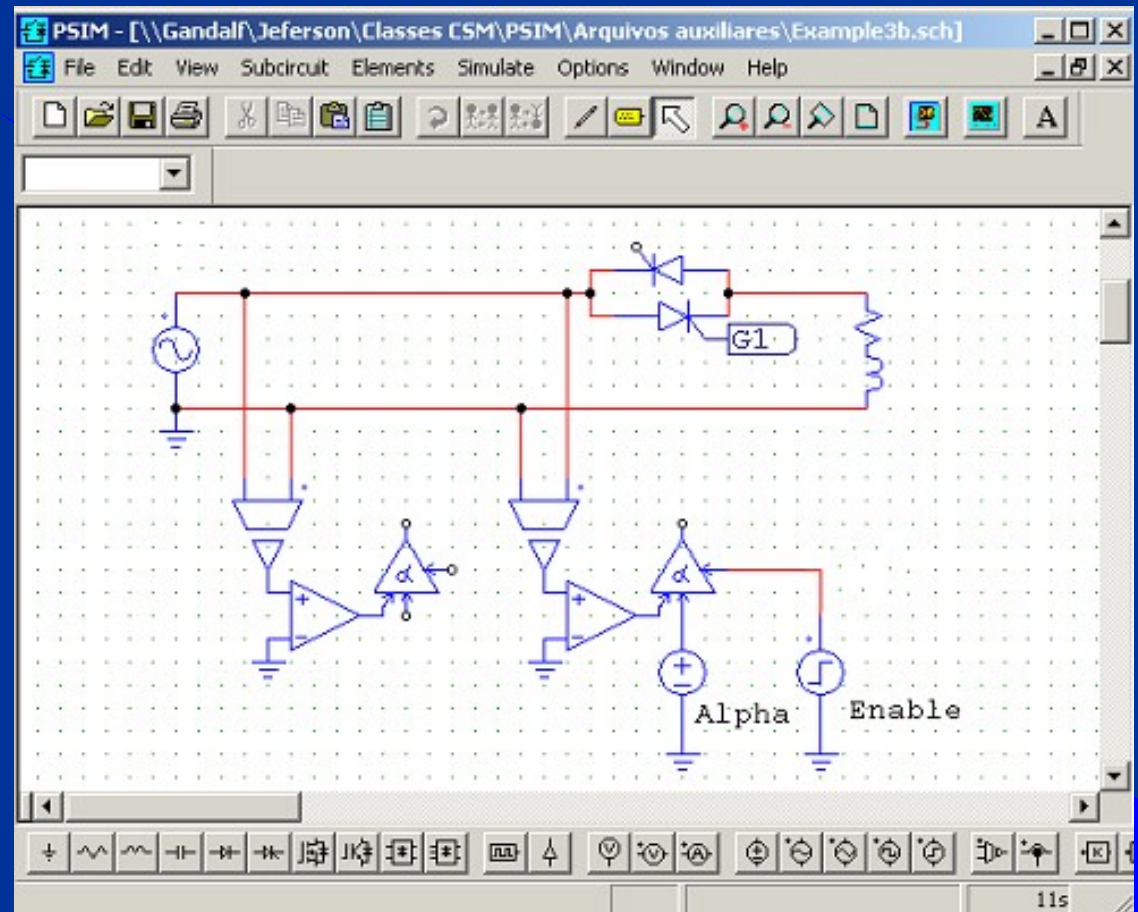
# Example 2: Voltage Controller


Create the alpha controller for the other  
*Thyristor.*

Insert a  
***Voltage  
Sensor, a  
Comparator  
and an Alpha  
Controller***  
block.


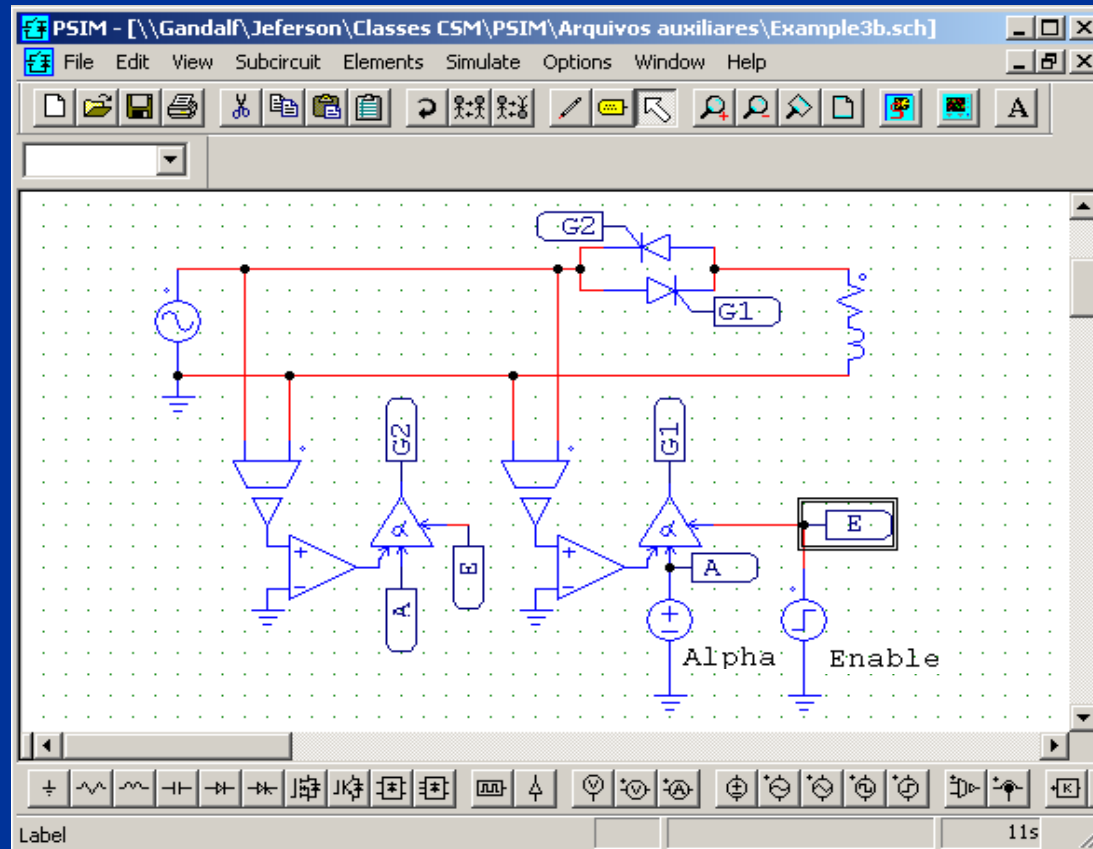
# Example 2: Voltage Controller


Use *Labels* for the *Enable* signal (*E*), Alpha signal (*A*) and *Gate* signal for *Thyristor 2* (*G2*).






# Example 2: Voltage Controller

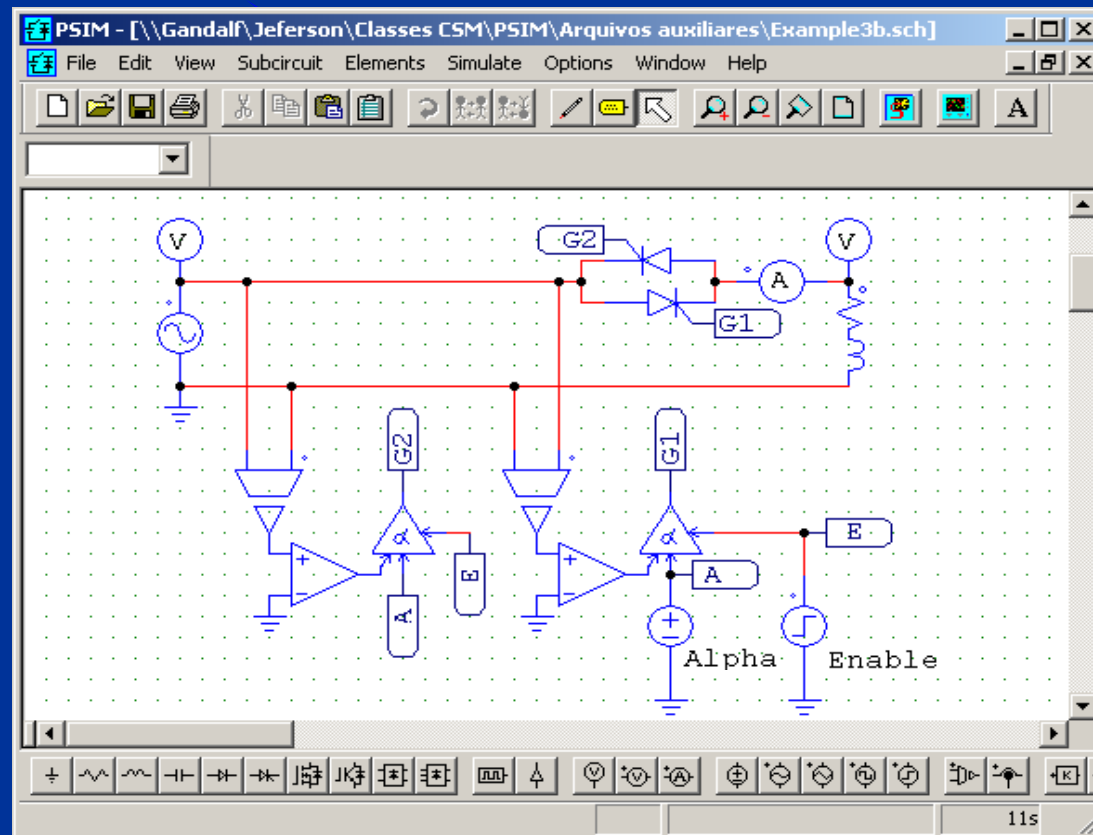**Insert an input *Voltage Probe* ( $V_i$ ), an output *Voltage Probe* ( $V_o$ ) and an output *Current Probe* ( $I_o$ ).**



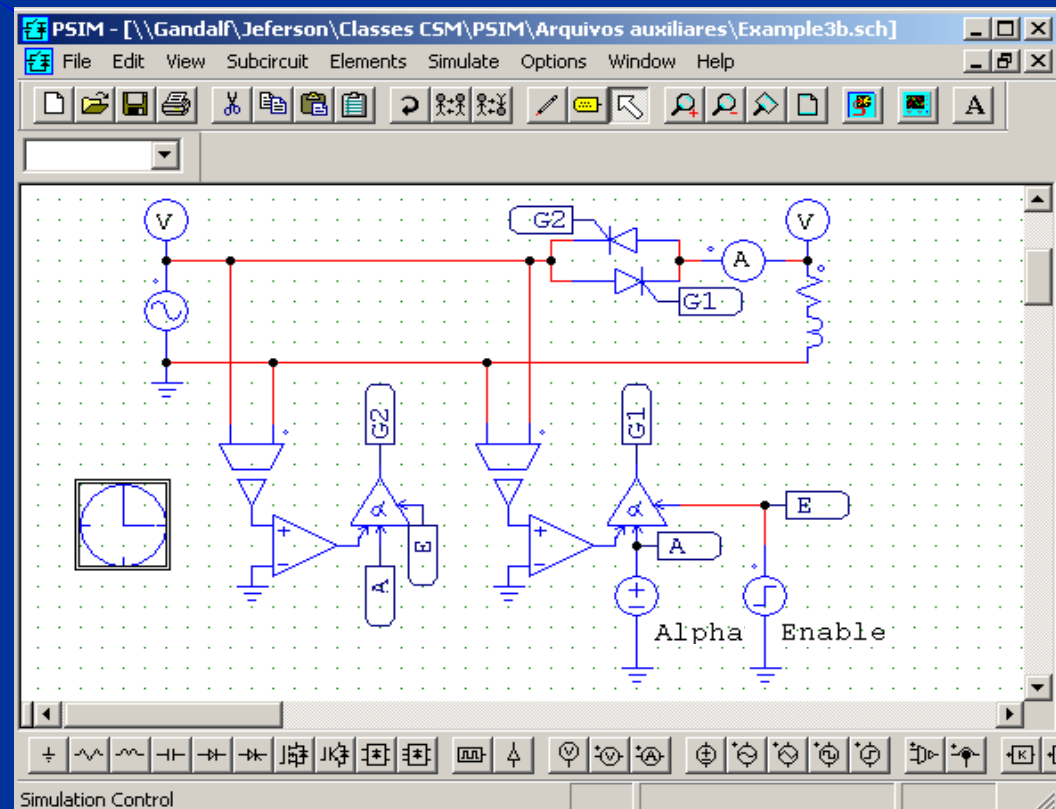
# Example 2: Voltage Controller

Insert a *Simulation Control* block. Set the simulation time to 50 mili-seconds




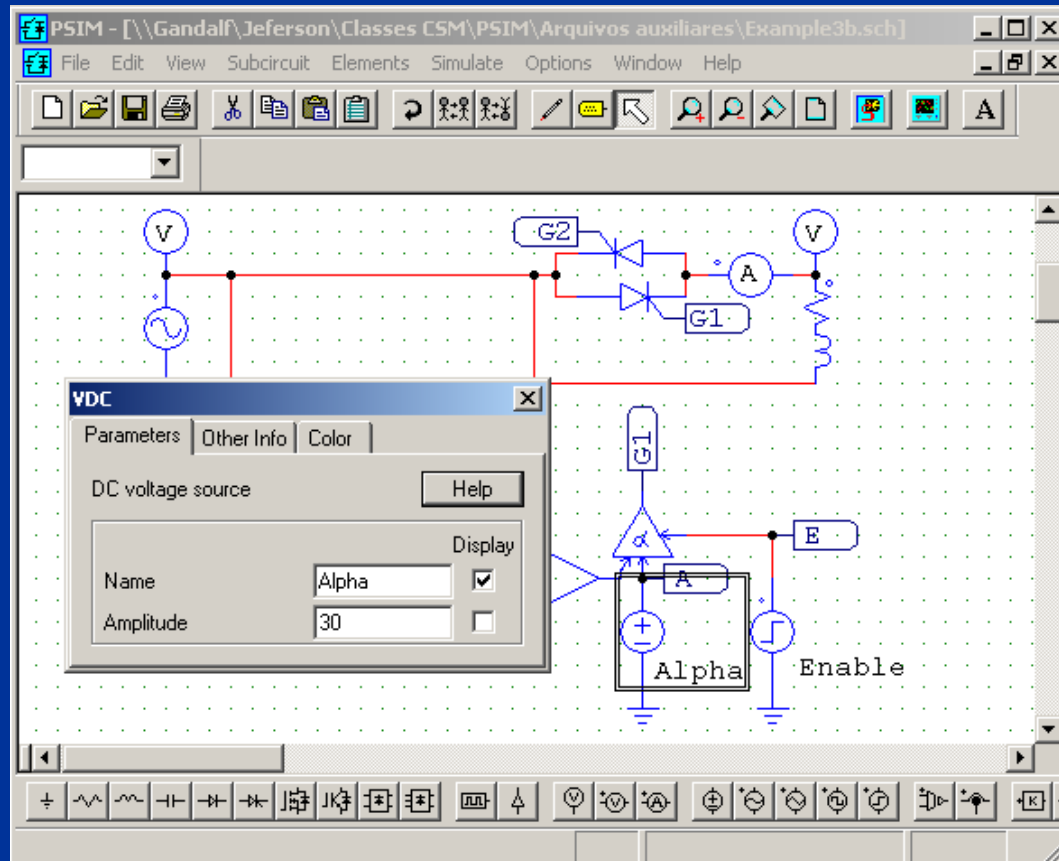**Set all the parameters values. Set the *Alpha* angle to 30°.**




# Example 2: Voltage Controller

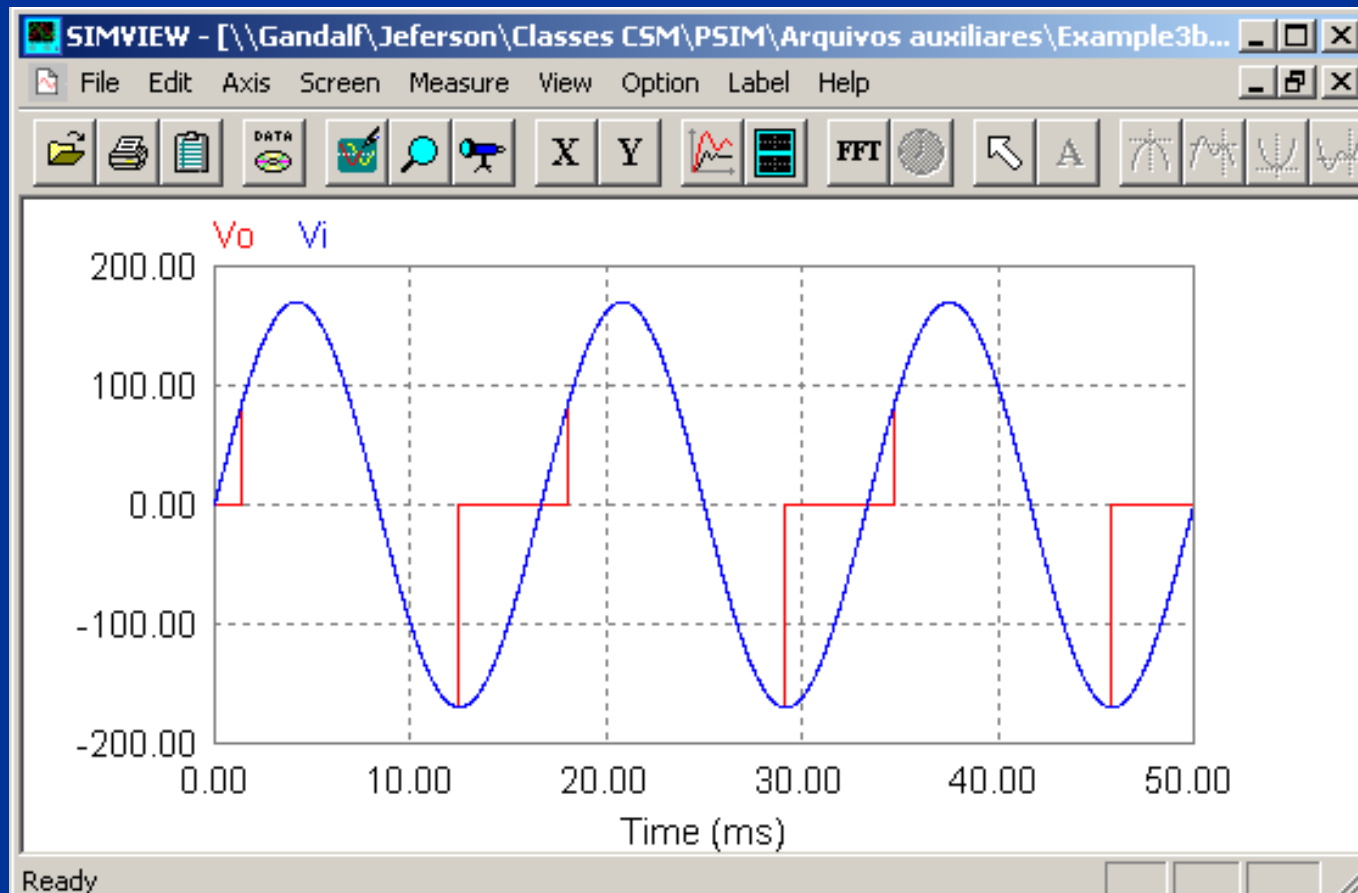**Run the Simulation. Plot  $V_i$  and  $V_o$ .**




# Example 2: Voltage Controller

**Add a new *Screen* and plot  $I_o$ .**

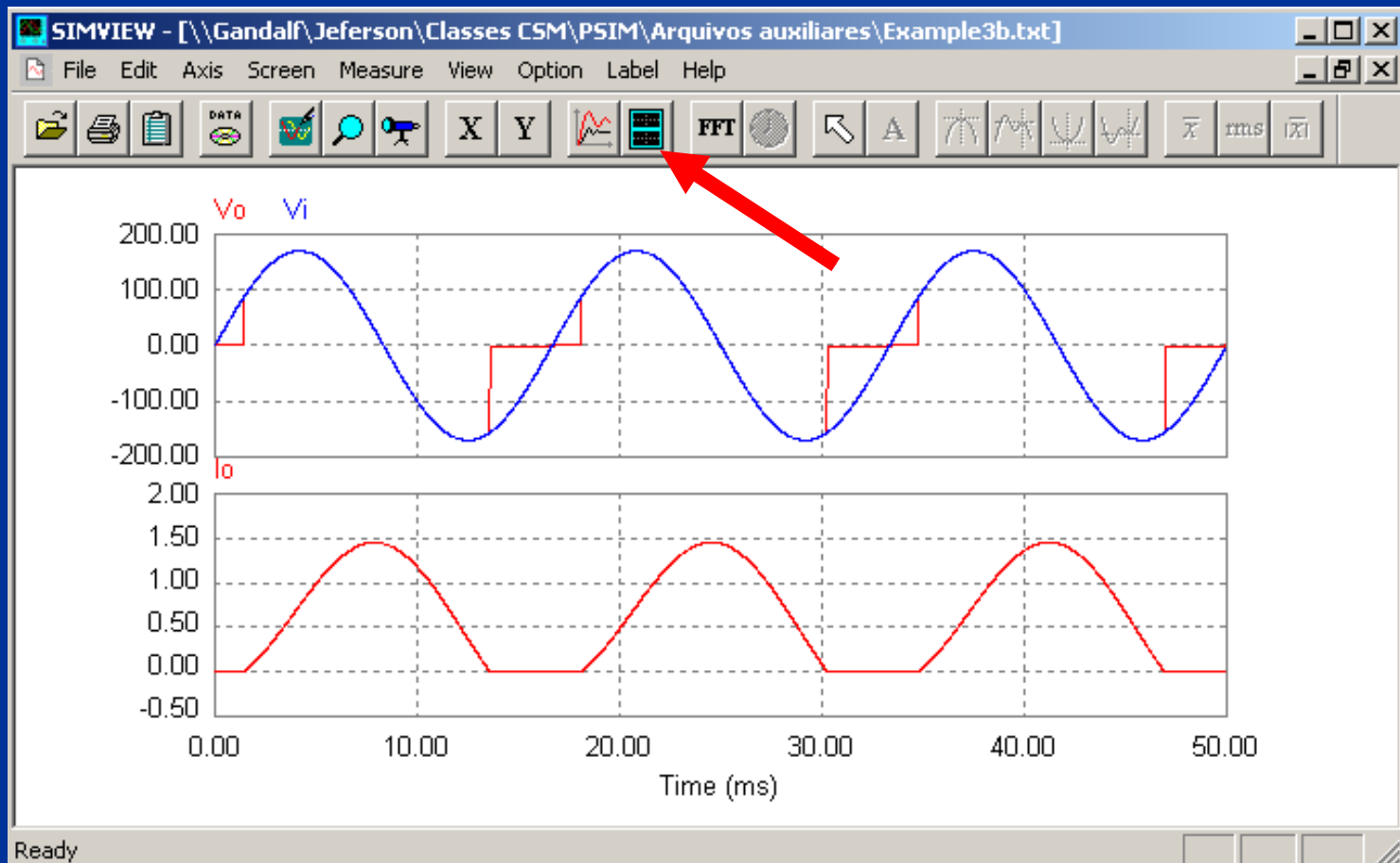


# Example 2: Voltage Controller

Other tools: *FFT* and *AVG*.

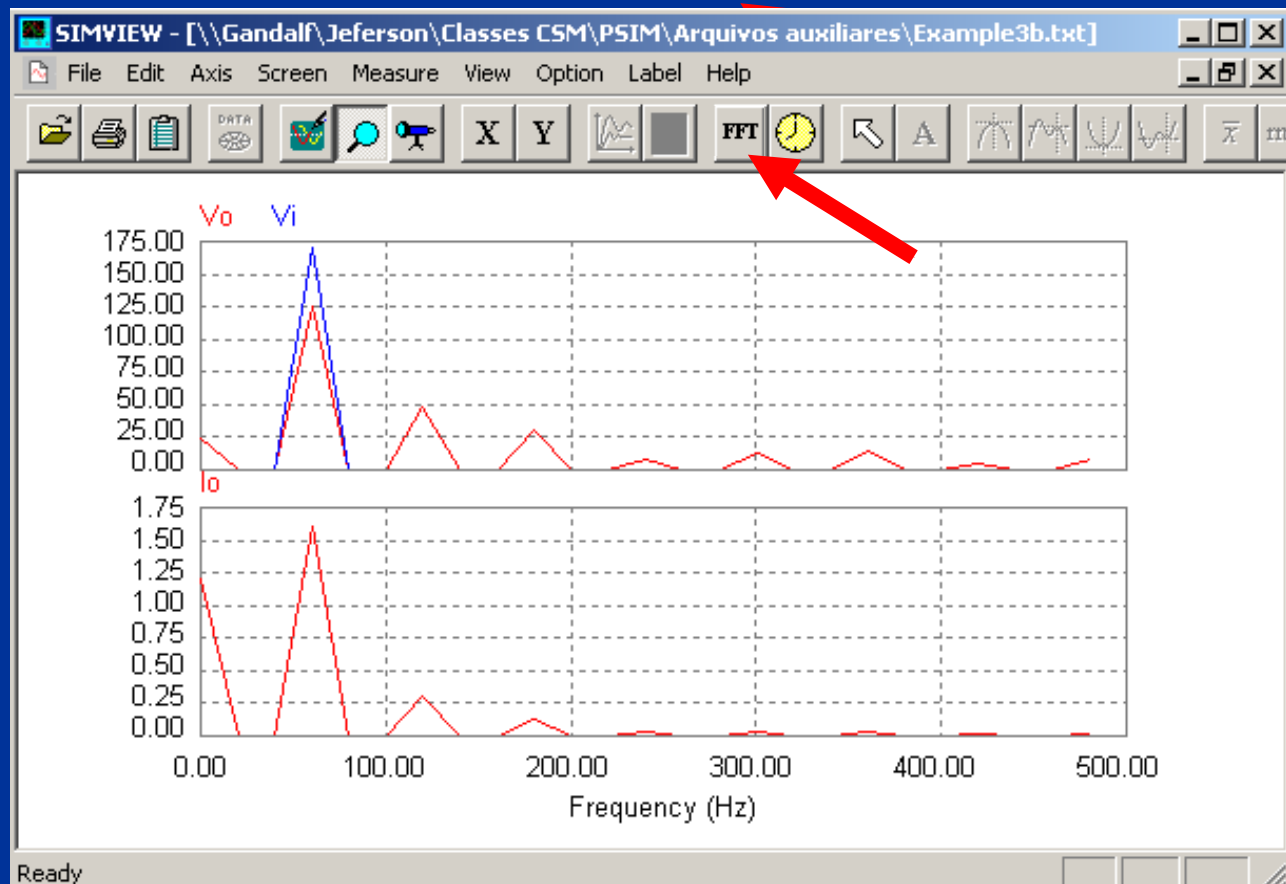

# Example 2: Voltage Controller


Other tools: *FFT* and *AVG*.

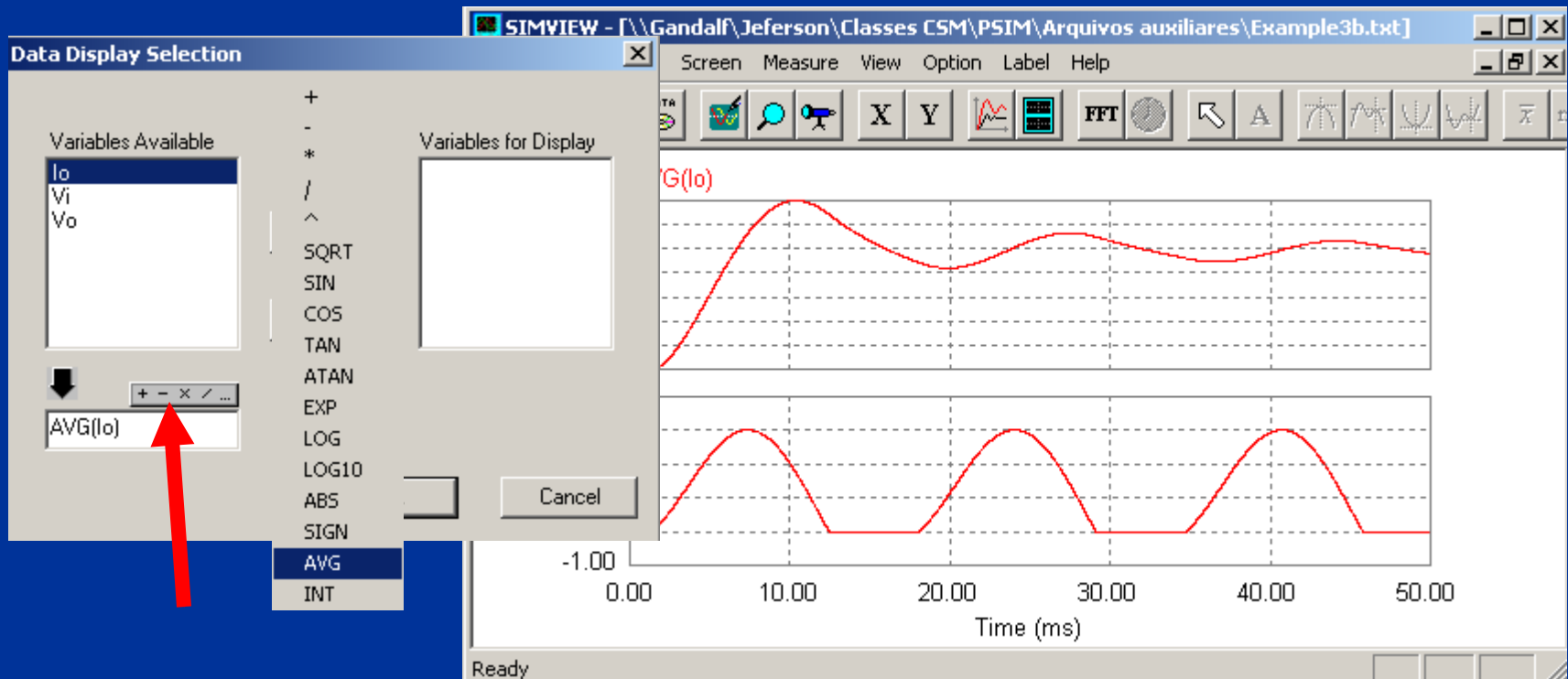


Run the circuit for *Alpha* equals to  $60^\circ$  and  $90^\circ$ .

## Example 2: Voltage Controller

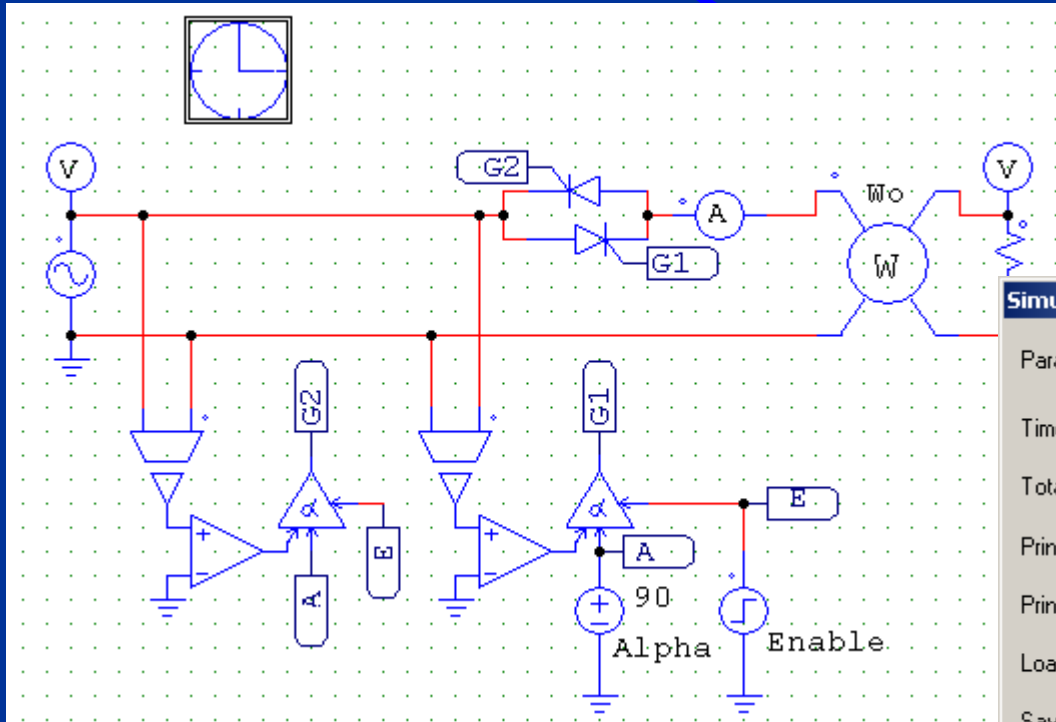**Additional measurements: load power, RMS current and power factor. (Example 5-2; Hart; pg 170)**



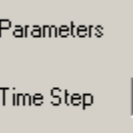**Add a *Watt Metter* from  
*Elements > Other  
> Probes > Watt  
Metter***



**Simulation Control**

Parameters Help

Time Step

Total Time

Print Time

Print Step

Load Flag


Save Flag

# Change the *Time Step*, *Total Time* and *Print* *Step*



# Example 2: Voltage Controller

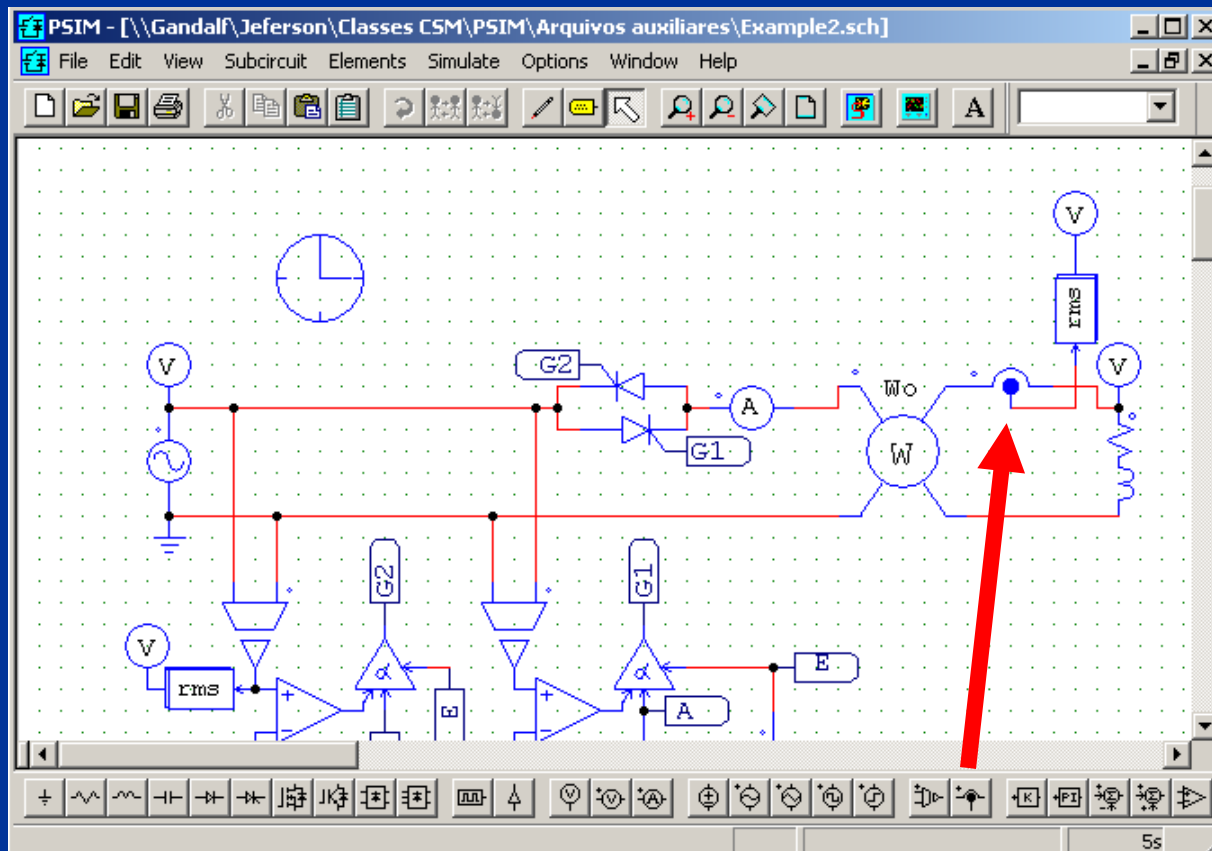**Additional measurements: load power, RMS current and power factor.**



**Add a *Current Sensor* and two *RMS* blocks from *Elements > Control > Computational Blocks > RMS***


**Add *Voltage Probes* to measure the RMS values**

# Example 2: Voltage Controller

**Additional measurements: load power, RMS current and power factor.**

$$\text{PF} = \frac{P}{S} = \frac{P}{V_{i,\text{rms}} \cdot I_{i,\text{rms}}} = \frac{147}{120 \cdot 2.71} \cong 0.45$$


## Example 3: Semiconverter

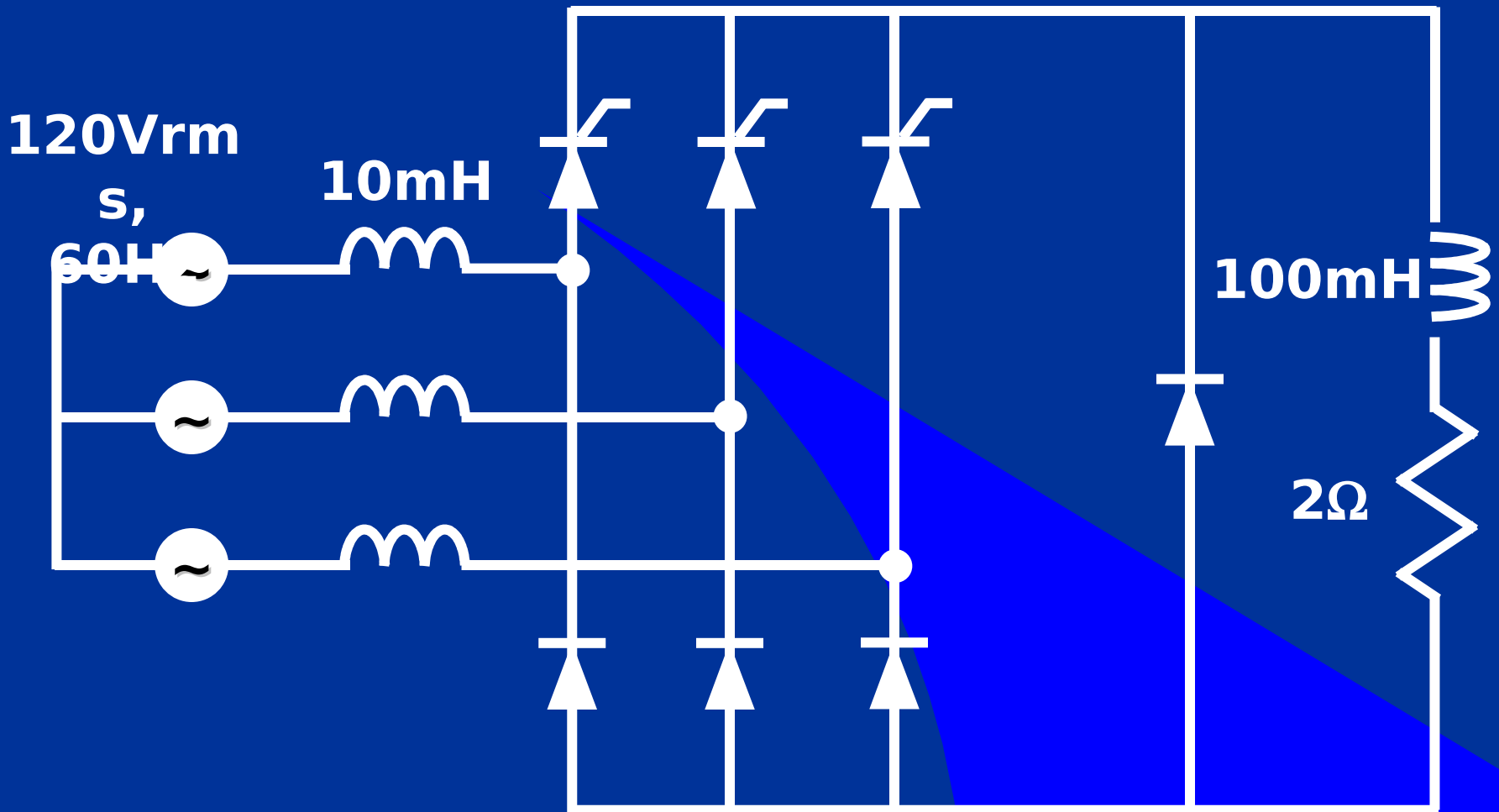

# Example 3:

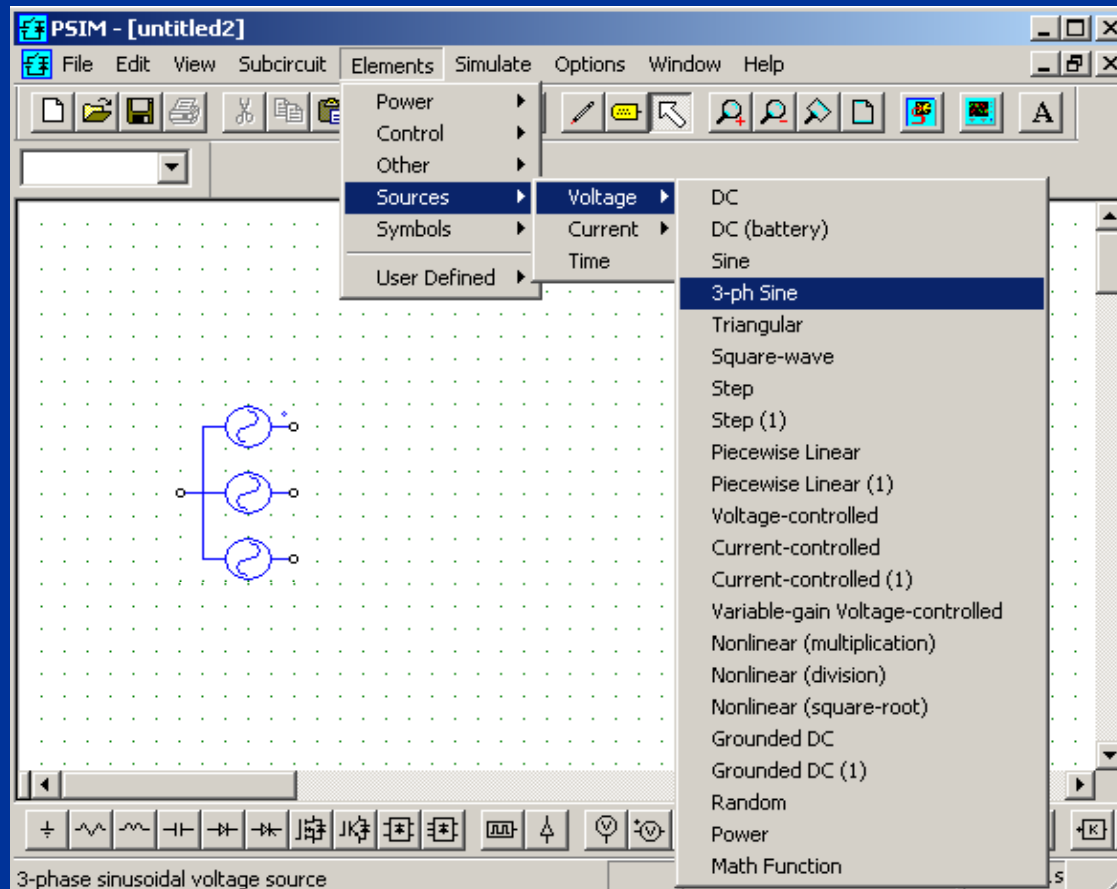
## Semiconverter

Create a new circuit. Insert a *Three-Phase Voltage Source*.



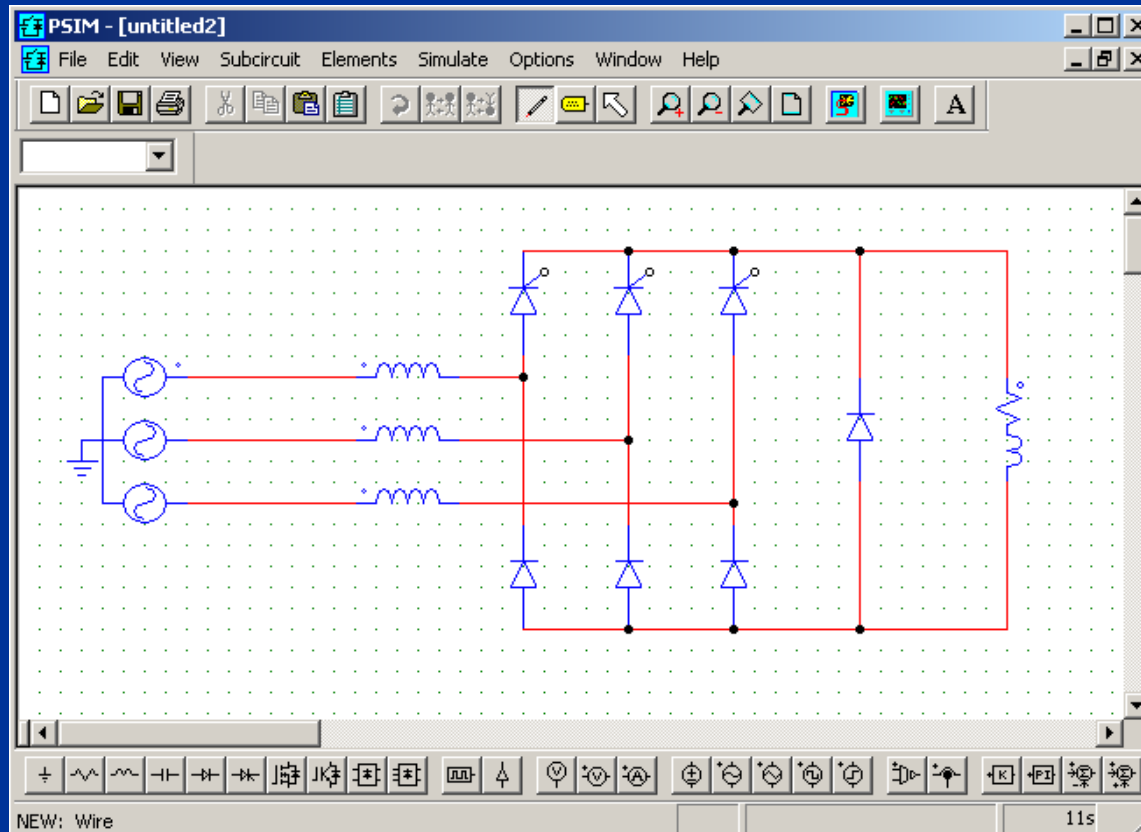
# Example 3: Semiconverter

Insert all the other power elements and  
connect them.



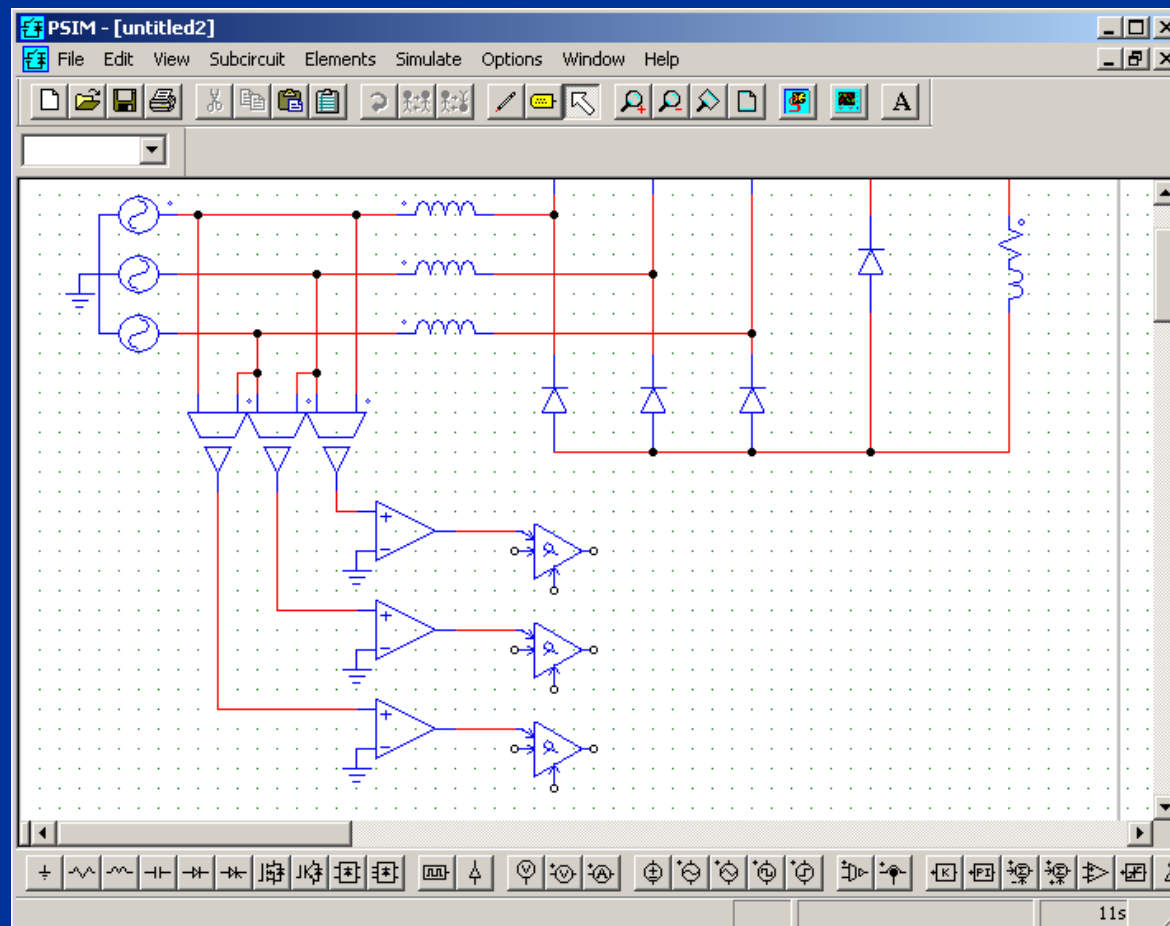
# Example 3: Semiconverter Insert and connect the *Alpha Controllers*.



# Example 3:
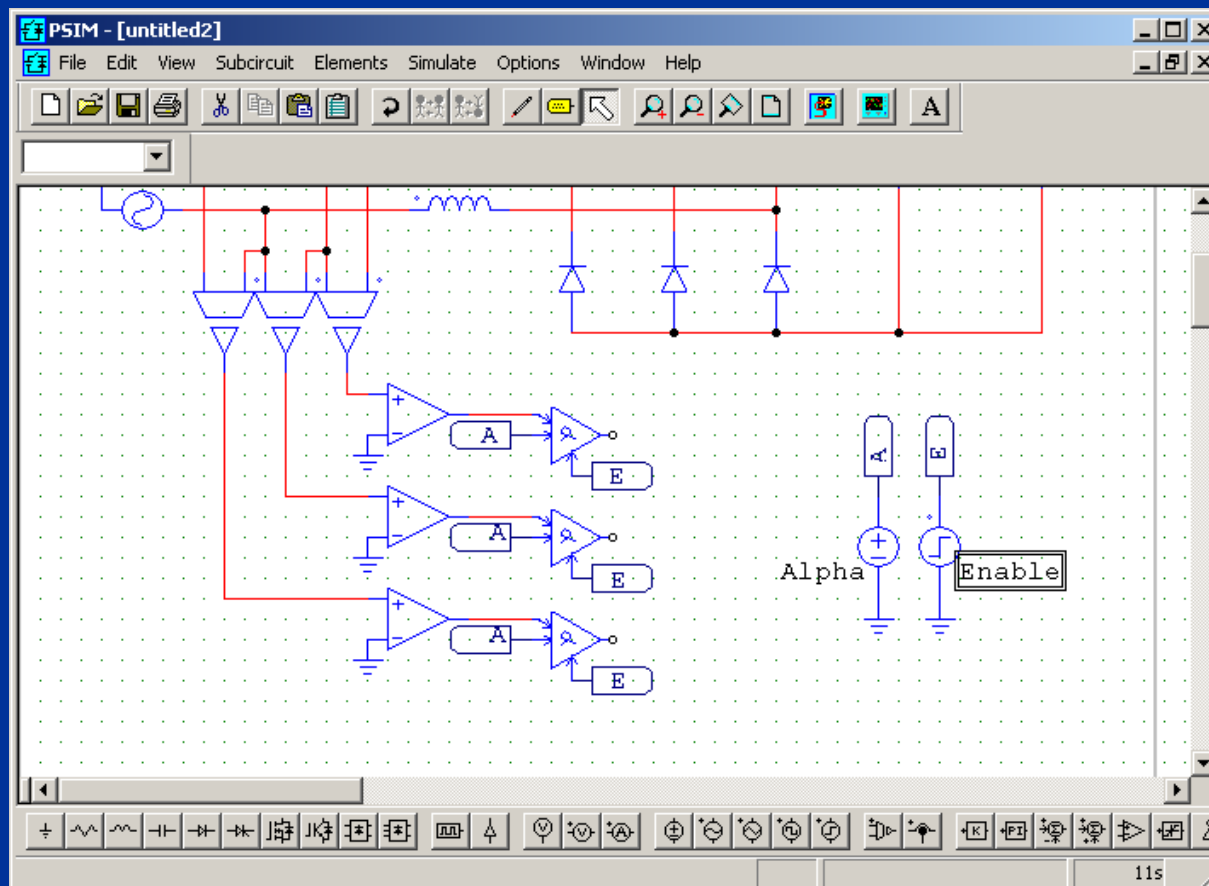
## Semiconverter


Insert the Sources for the angle *Alpha* and for the *Enable* signal.


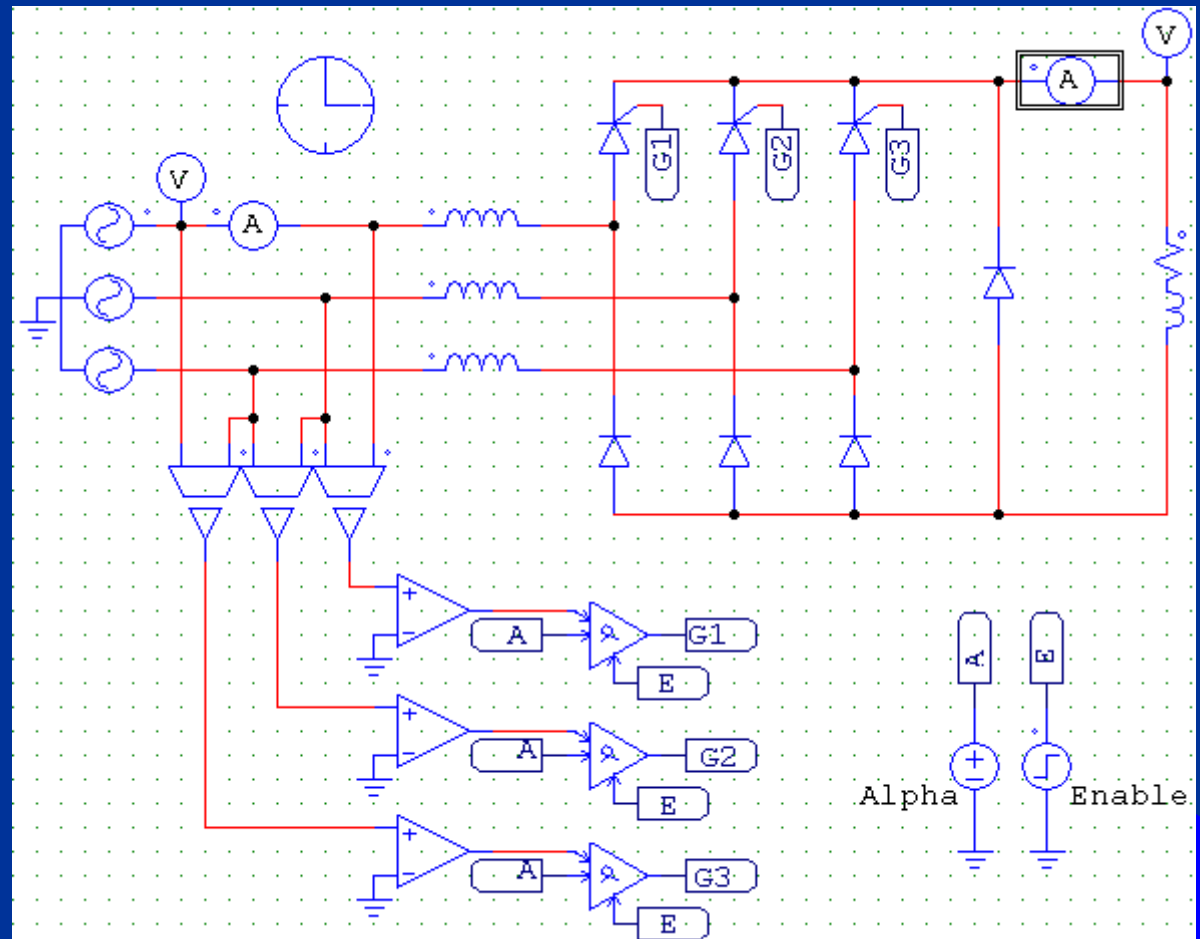
## Example 3:

Connect the Semiconverter Gate signals, insert a *Simulation Control* (50 ms) and set all the parameters.


Insert an input *Voltage Probe*, an output *Voltage Probe*, an input *Current Probe* and an output *Current Probe*.




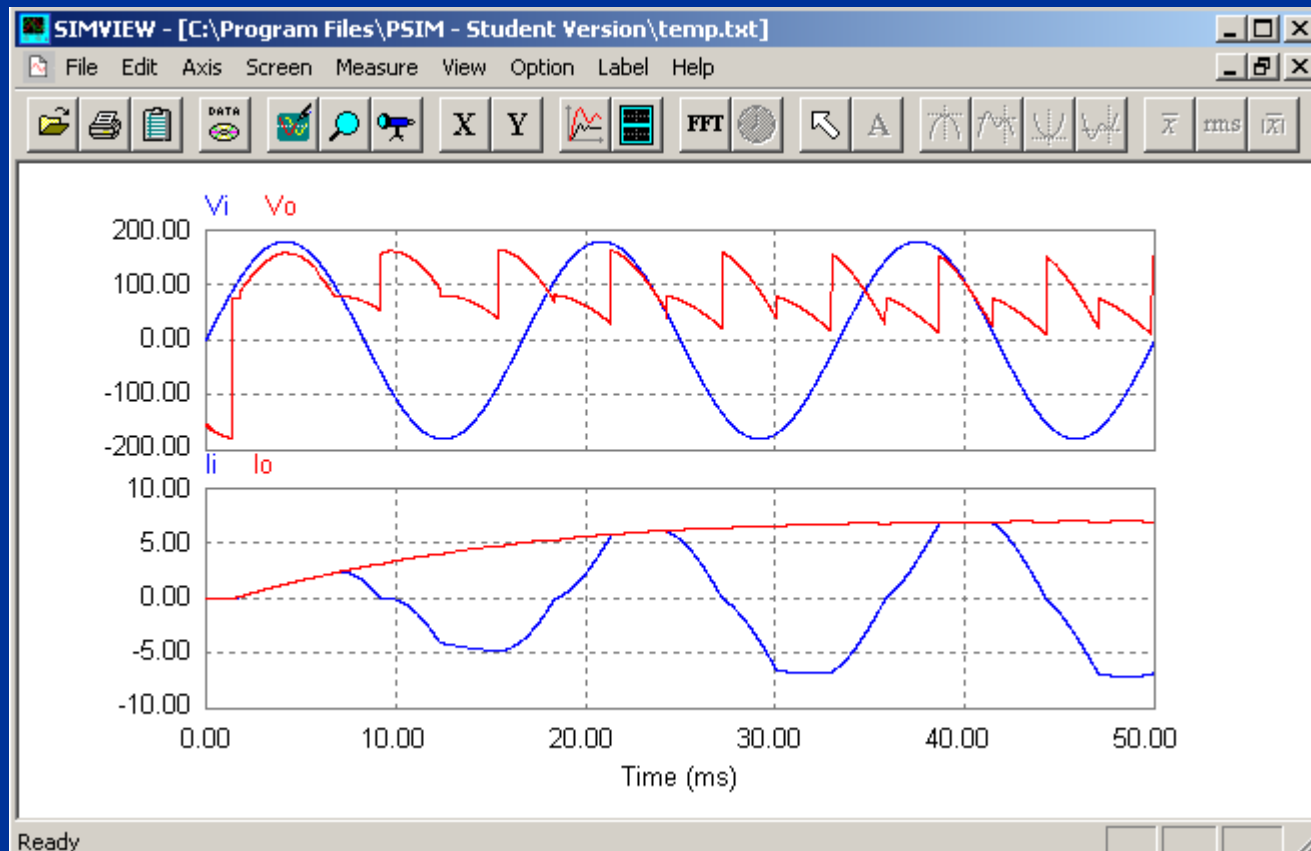
# Example 3: Semiconverter

Run the circuit for *Alpha* equals to 30, 60 and 90 degrees. Check the results.



# Example 3: Semiconverter

## **Exercise:**

**Implement the additional measurements for this circuit: THD, load power, RMS current and power factor.**

**See Ex. 5.9; Rashid; pg 156**